 



Homework 7: Logical Effort

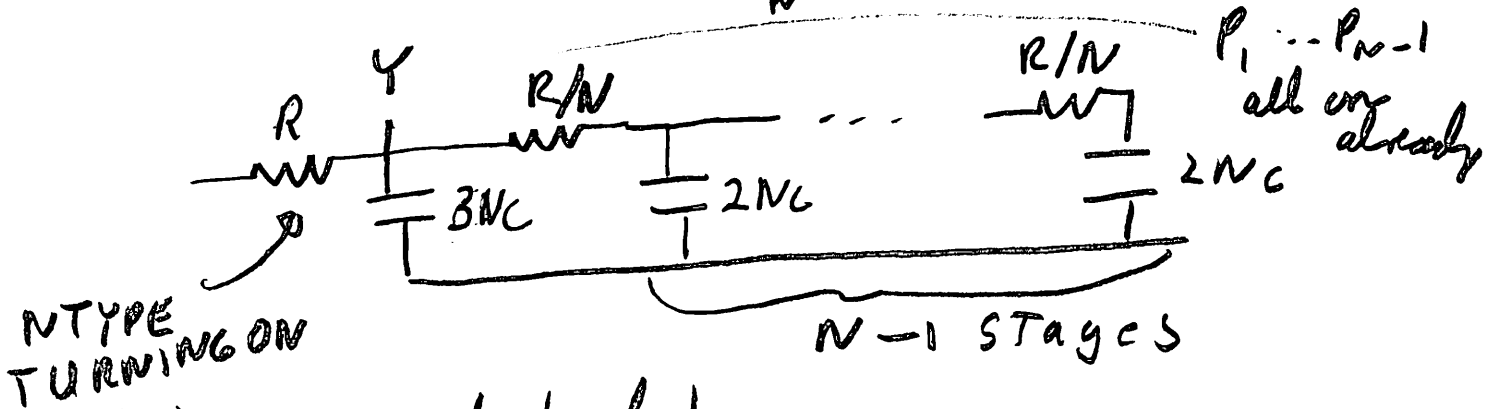1. Book: 4.4 Worst case parasitic delay Elmore model for n-input NOR gate



Total of  $2N + N \cdot 1C$   
on  $Y = 3N$

Worst case Fall Time:  $I_1 - I_N$  all at 0  
 $I_N$  goes from 0 to 1



N TYPE  
TURNING ON

Elmore model delay


$$R * \left( \sum_{i=1}^{N-1} 2NC + 3NC \right) = R(2N^2C + NC)$$

$$= (2N^2 + N)RC$$

Worst Case Rise Time

$I_n - I_{n-1}$  at  $\phi$

$I_N$  goes from 1 To 0

 

$$\frac{R}{N} 2nC + 2 \frac{R}{N} 2nC + \dots + \frac{(N-1)R}{N} 2nC + R 3nC$$

$$= R 2c (1 + \dots + N-1) + 3NRC$$


$$= R 2c \left( \frac{(N-1)N}{2} \right) + 3NRC$$

$$= RC(N^2 - N) + 3NRC$$


$$= RC(N^2 + 2N)$$

Fall Time is worst

 
202. Fig. 1.18 in the book (p. 12) shows a compound gate. Do the same for this circuit as for Problem 1.



 Fall Time: assume  $A, C = 1, D = 0$ ;  $B$  goes from 0 to 1



To get  $Y$  sum

 


$$\frac{R}{2} \times 2C + \left(\frac{R}{2} + \frac{R}{2}\right) 14C = 15RC$$

Rise Time: assume  $A = 0$

$$B = 0$$

$$D = 1$$

C goes from 1 To  $\phi$

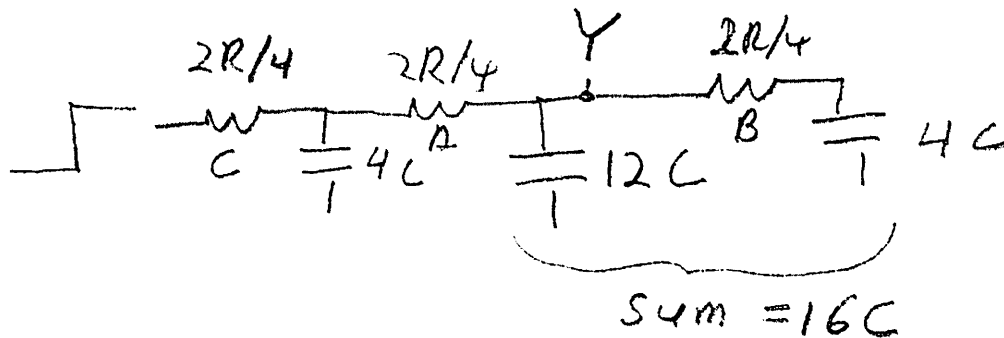

$$\frac{2R}{4} 4C + \frac{4R}{4} (16C) = 18RC$$


So Rise Time is worse here

Rise Time: assume  $A = 0$

$$B = 0$$

$$D = 1$$

C goes from 1 To  $\phi$

 

$$\frac{2R}{4} 4C + \frac{4R}{4} (16C) = 18RC$$


So Rise Time is worse here

# Alternative Worst Case Falling

$C, D = 0 \rightarrow 1$  (CD)

$B = 0$


$A = 1$

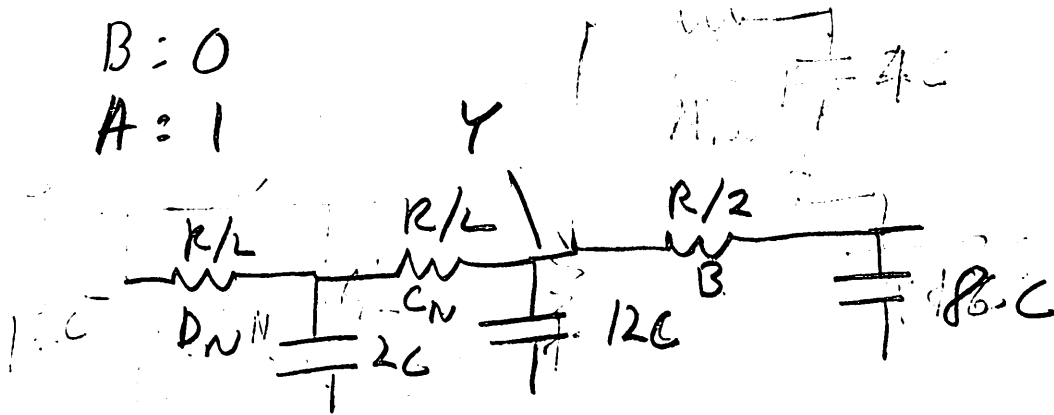

$$\frac{R}{2} \times 2C + R(12 + 80)C = 21C$$


# Worst Case RISING

$A, C = 0 \rightarrow 1, B, D = 0$

 


$$\frac{R}{2} 8C + R 16C = 20RC$$

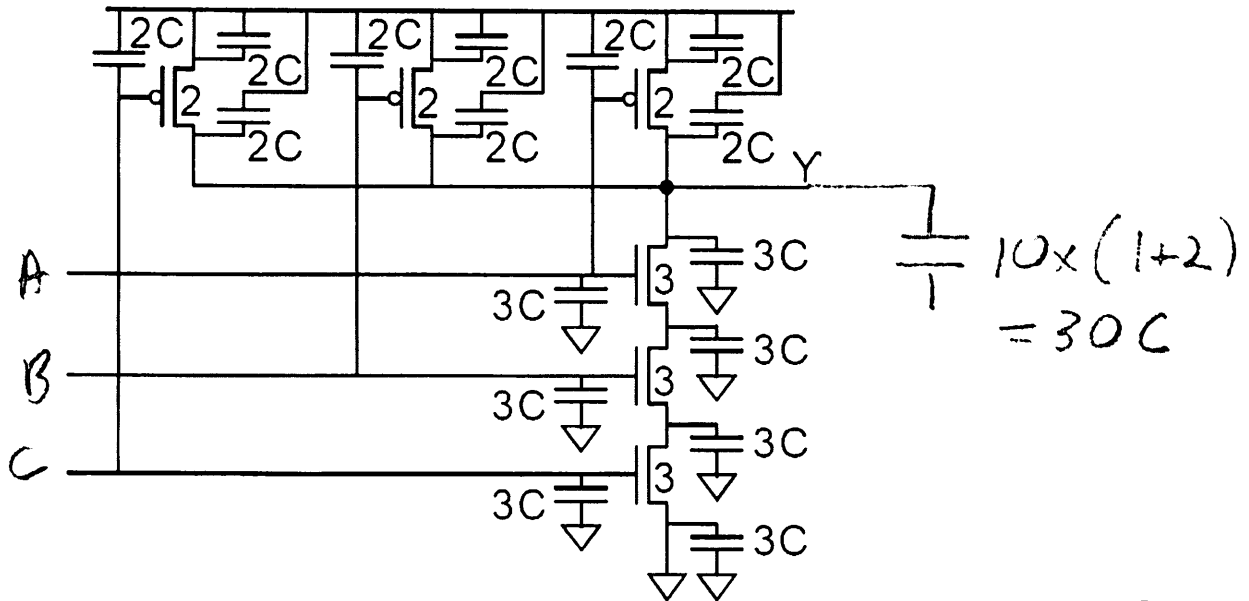20 3. Build an Elmore model for both rise and fall times for a 3 input NAND as described in Fig. 4.7 on page 148 driving 10 inverters sized as in Fig. 4.6 (i.e. p has a k of 2, n type has a k of 1).



 
Rise Time - one of p's Turns on, one n Turns off  
 - worst case is if A+B are left on



$$= 45C$$

$$45RC$$

 
Fall Time: worst if C is last TS switch on



$$\frac{R}{3} 3C + \frac{2R}{3} 3C + \frac{R}{3} 3C = 4RC$$

 4. Book.Book: 4.5 but for a 3 input NOR and compare to a 3 input nand as in Fig. 4.21

For a 3 input NOR,  $p=3$  and  $g=7/3$  from tables.



5. Book 4.6

Unit inverter has 3 units of capacitance (2 from pmos, 1 from nomos). For 4X inverter nmos is now 4 and pmose is  $2 \cdot 4 = 8$  for a total of 12.

Changing the size does not change the logical effort or parasitic delay from that of the 1X

6. Book 4.8

Drive is defined as  $C_{in}/g$ ,

- For unit inverter  $g$  is 1,  $C_{in}$  is 3 units (page 159), and  $C_{in}/g = 3/1 = 3$ . This corresponds to "1 unit of drive" For 4x unit cap  $g$  unchanged,  $C_{in}$  is 4, making  $x = 4/1 = 4$
- NAND2 has a  $g$  of  $4/3$ . If the NAND also has 3 units of 1 nput cap, then  $C_{in}/g = 3/(4/3) = 9/4$ . But if a "unit inverter with a  $C_{in}/g$  of 3" has unit drive, then this inverter is  $9/4/3 = 3/4$  units of drive.