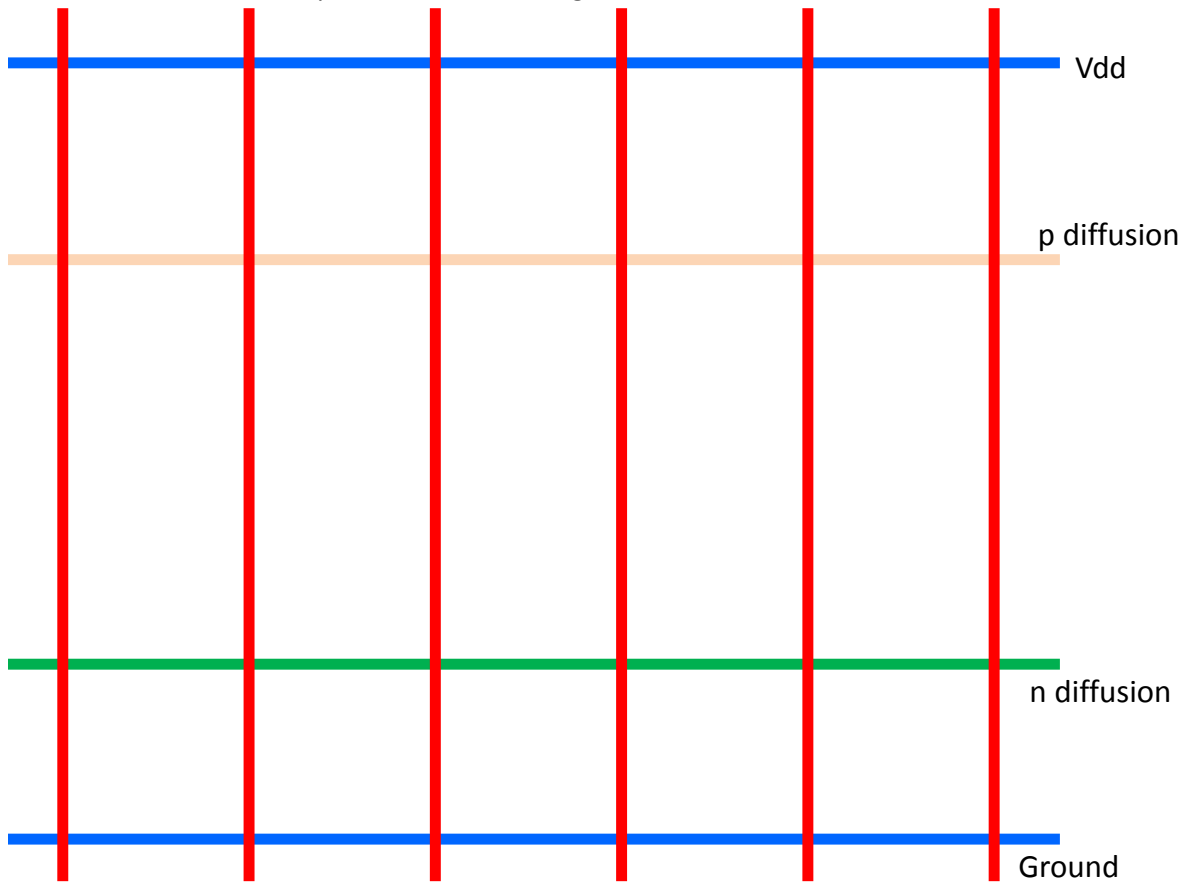


Homework 3

1. (40) For the function $\text{not}((A+B)(C+D)+EF)$ draw a transistor-level schematic, stick diagram, and estimate area. The web site has additional copies of a blank stick figure sheet.



3. (30) Annotate the stick figure below to show as many design rules as possible (use the set of rules on book's inside cover).

