

# Introduction to CMOS VLSI Design

## Logical Effort Part B

Original Lecture by Jay Brockman

University of Notre Dame Fall 2008

Modified by Peter Kogge Fall 2010,2011,2015, 2018

Based on lecture slides by David Harris, Harvey Mudd College


<http://www.cmosvlsi.com/coursematerials.html>

Logical Effort B

Slide 1
 
## Review: Motivating Example

- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the *decoder* for a 16x32 register file.



- ❑ Decoder specifications:
  - 16 word register file
  - Each word is 32 bits wide
  - Each file bit presents load of 3 unit-sized transistors
  - Both true & complementary address inputs  $A[3:0]$  available
  - Each address input may drive 10 unit-sized transistors
- ❑ Ben needs to decide:
  - How many stages to use in decoder driver output buffers?
  - How large should each gate be?
  - How fast can decoder operate?


Logical Effort B

CMOS VLSI Design

Slide 2
 
## Review: Ideal Gate Delay $\tau$

- Imagine *ideal unit inverter* (no parasitic diffusion capacitance & unit on resistance) driving *identical inverter*



$$\tau = 3RC = \text{Ideal Inverter Delay}$$

Logical Effort B

CMOS VLSI Design

Slide 3

## Review: Linear Delay Model

$$\text{delay } d = p + f = p + hg$$

Prior delay had two parts

- $p$ : **Parasitic delay** due to internal diffusion capacitance of gate
  - $3RC$  for inverter
  - Independent* of load = sum of diffusion caps
- $f$ : **Effort delay** due to load capacitance of gates being driven
  - $3hRC$  when driving  $h$  unit inverters
  - Proportional* to total load capacitance
- $= h \cdot g$  if driving *identical* circuits (copies of itself)
  - $h$  = # of copies of gate (also called "**Fanout**")
  - $g$  = "**Logical Effort**" (function of gate complexity)
    - $3RC$  for inverter

Logical Effort B

CMOS VLSI Design

Slide 4

## Review: Normalized Linear Delay

- Remember
  - $3RC$  = parasitic delay of unit inverter
  - $3RC + 3hRC$  = delay if driving  $h$  inverter copies
  
- **Normalized delay**: divide delay by  $3RC$ 
  - Measure of how much “slower” a circuit is than an inverter
  - =  **$1 + h$**  for inverter driving  $h$  identical inverters


Logical Effort B

CMOS VLSI Design

Slide 5

 
## Determining Logical Effort

- **Logical effort  $g$** : ratio of input capacitance of a gate to input capacitance of an inverter *delivering the same output current* (pullup/down resistance).
- Measured from delay vs. fanout plots
- Or estimate by counting transistor widths
  - **AND divide by 3 to “normalize”** to unit inverter




$$C_{in} = 3$$

$$g = 3/3$$

 

$$C_{in} = 4$$

$$g = 4/3$$

 

$$C_{in} = 5$$

$$g = 5/3$$

Question: does  $g$  change if we scale all the transistors wider?

Logical Effort B

CMOS VLSI Design

Slide 6

# Summary: (p.156)

Gate Type	Number of inputs												
	1	2	3	4	N								
Inverter	3	1	1										
NAND		4	2	4/3	5	3	5/3	6	4	6/3	N+2	N	(N+2)/3
NOR		5	2	5/3	7	3	7/3	9	4	9/3	2N+1	N	(2N+1)/3
TriState/mux	2	2	4	2	6	2	8	2			2N	2	
XOR, XNOR		4	4,4	6	6,12,6	8	8,16,16,8						

(x,y,z) = Input Cap, p, g

*All inputs are **not** the same!*

**Parasitic:** delay driving 0 load (divided by 3RC)

**Logical effort:** Input Cap of gate / Input Cap of inverter of same current

Logical Effort A

CMOS VLSI Design

Slide 7

# Delay Plots


$$d = f + p$$

$$= gh + p$$

*slope* *intercept*

Lets take our inverter:

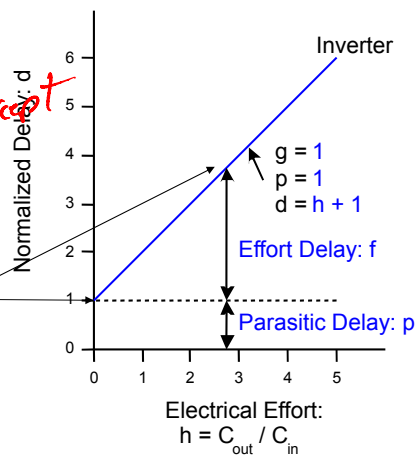- $d = h + 1$
- $p = 1$  (y-intercept)
- $g = 1$  (slope)



What does "Normalized Delay" mean to designer?

Logical Effort B

CMOS VLSI Design



Slide 8

# 2 input NAND

$$d = f + p$$

$$= gh + p$$

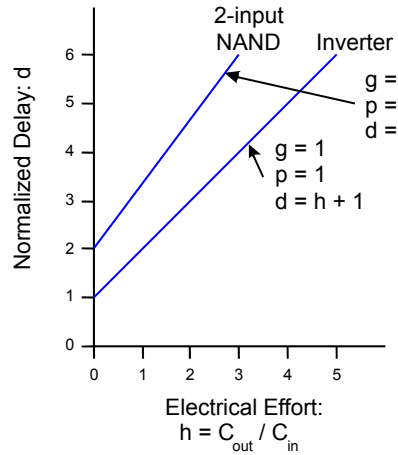 Remember we normalize by unit inverter 3RC



Logical Effort B



CMOS VLSI Design

Slide 9

# More 2 input NAND

$$d = f + p$$

$$= gh + p$$

 
 


Logical Effort B

CMOS VLSI Design

Slide 10

# 3 Input NAND

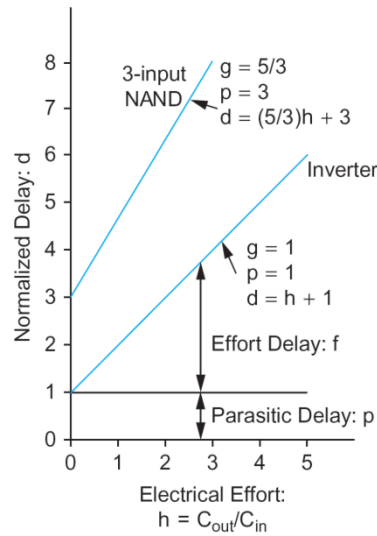 


Logical Effort B

CMOS VLSI Design

Slide 11
 
## Eg: Ring Oscillator (p.158)

- Estimate the frequency of an N-stage ring oscillator
  - N odd



Each Stage:

- Logical Effort:  $g = 1$
  - Electrical Effort:  $h = 1$
  - Parasitic Delay:  $p = 1$
  - Stage Delay:  $d = (1 + h) = (1 + 1) = 2$
  - Total delay:  $Nd = 2N$  (normalized)  
 $= 2D\tau$  (in seconds)
  - Overall Frequency:  $f_{osc} = 1/(2N\tau)$
- 31 stage ring oscillator
- 65nm process (3ps delay) = 2.7GHz
  - 0.6  $\mu\text{m}$  process ~ 200 MHz


Logical Effort B

CMOS VLSI Design

Slide 12
 
## Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g =$

Electrical Effort:  $h =$

Parasitic Delay:  $p =$

Stage Delay:  $d =$


Logical Effort B

CMOS VLSI Design

Slide 13
 
## Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g = 1$

Electrical Effort:  $h = 4$

Parasitic Delay:  $p = 1$

Stage Delay:  $d = 5$

The FO4 delay is approximately

- 200 ps in 0.6  $\mu\text{m}$  process
- 60 ps in a 180 nm process
- $f/3$  ns in an  $f$   $\mu\text{m}$  process

Logical Effort B

CMOS VLSI Design


Slide 14

# Drive (p.159)

- ❑ Most libraries have multiple versions of common gates
  - Named **<gate-type>\_#x**
- ❑ Versions differ by “size” of transistors
  - Denoted by **#** in name
  - Called the gate version’s **drive**
    - Relative to unit inverter
- ❑ **Drive x** =  $C_{in} / g$
- ❑ Thus delay =  $C_{out} / x + p$
- ❑ Question: what’s speed difference between
  - nand2\_1x
  - nand2\_3x

(p. 160)

Figure 4.25 Artisan Components cell library datasheets. Reprinted with permission. (180 nm process)

 




(p. 160)

Figure 4.25 Artisan Components cell library datasheets. Reprinted with permission. (180 nm process)

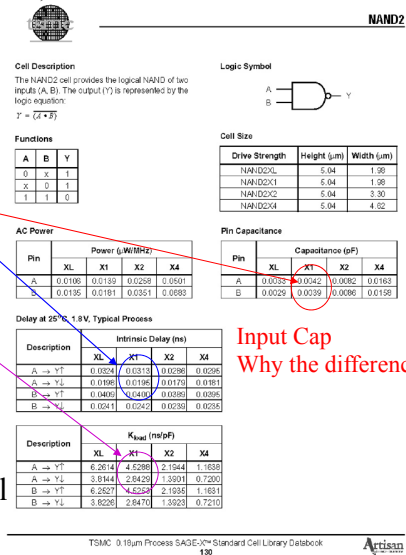- Lets look at A input
- Parasitic delay =  $(31.3+19.5)/2$   
= 25.4ps
- $C_{in} = 4.2fF$
- $K_{load} = (4.53+2.84)/2$  ns/pF  
= 3.69 ns/pF  
= 3.69 ps/fF
- $t_{pd} = 25.4 + 4.2*3.69$  ps  
= 25.4 + 15.5\*ps
- Normalizing by inverter 12.4ps
  - $p = 25.4/12.4 = 2.05$
  - $g = 15.5/12.4 = 1.25$ 
    - versus  $4/3 = 1.33$  from model



Input Cap  
Why the difference?

Logical Effort B

CMOS VLSI Design

Slide 17

(p. 161)

## Limitations to Linear Delay Model


- ❑ Input & output slopes:
  - not square
- ❑ Input arrival times: complex interactions
  - when 2 or more inputs change at same time
- ❑ Velocity Saturation:
  - We assume N transistors in series must be N times wider
  - But series transistors see less velocity saturation
    - & hence less resistance
- ❑ Voltage Dependencies:
  - $\tau \sim V * V_{DD} / (V_{DD} - V_T)^\alpha$
- ❑ Gate/Source Dependencies:
  - We assumed gate caps terminate on a fixed rail
  - In reality to “middle” of channel
- ❑ Bootstrapping:
  - Transistors have “gate to drain” capacitance
  - Causes input to output “lifting”

Logical Effort B

CMOS VLSI Design

Slide 18


# Bootstrapping

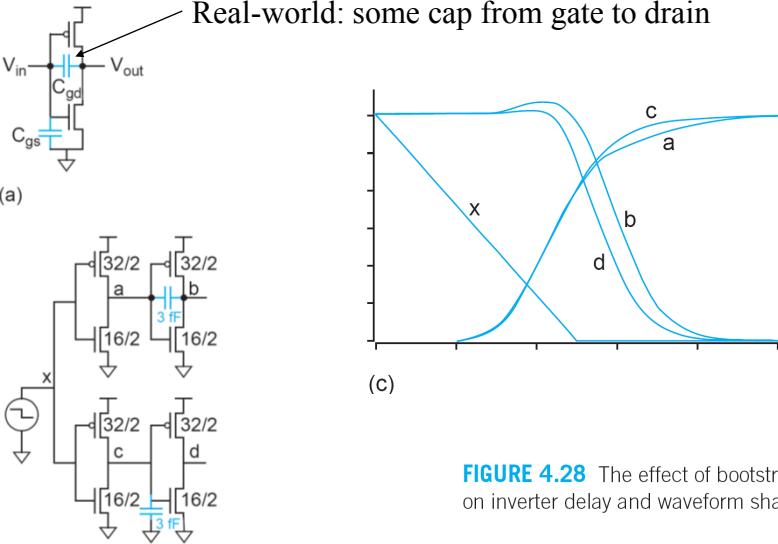

**FIGURE 4.28** The effect of bootstrapping on inverter delay and waveform shape

# Delay in Multi-Stage Circuits

## A Sample Multi Stage Circuit

 

Gate Type	Number of inputs												
	1	2	3	4	N								
Inverter	3	1	1										
NAND		4	2	4/3	5	3	5/3	6	4	6/3	N+2	N	(N+2)/3
NOR		5	2	5/3	7	3	7/3	9	4	9/3	2N+1	N	(2N+1)/3
TriState/mux		2	2		4	2		6	2			2N	2
XOR, XNOR			4	4,4	6	6,12,6		8	8,16,16,8				

$$(x,y,z) = \text{Input Cap, } p, g$$

Logical Effort B

CMOS VLSI Design

Slide 21

## Scaling Transistors

- ❑ What if all transistors in gate G got *wider* by k?
  - Denote as gate “G(k)”
- ❑ **Parasitic delay** of G(k): delay of unloaded gate
  - Diffusion capacitance increases by k
  - Resistance decreases by k
  - Result: *No change*
- ❑ **Effort delay**: ratio of load cap to input cap
  - If drive same # of G(k) as before, *no change*
  - If drive same # of G(1) as before, *decrease* by 1/k
  - If drive k times as many G(1), *no change*
- ❑ Result: **fanout** to type G(1) gates *increases by k*
- ❑ **YOU CAN DRIVE MORE GATES AT SAME SPEED!**
  - **OR DRIVE SAME GATES FASTER**

Logical Effort B

CMOS VLSI Design

Slide 22

## Design Question

- ❑ Given a signal path thru multiple gates
  - Of different types
  - And different #s on each output
- ❑ How do we select transistor scale factors?
  
- ❑ Answer: analyze/select “input capacitance”
  - And then adjust transistor scaling to give you that value

Logical Effort B

CMOS VLSI Design


Slide 23

## MultiStage Logic Networks

(p. 163)

### Relative Input Capacitance

(based on gate design & transistor size)

 

**FIG 4.29** Multistage logic network

$g_i$  = logical effort to drive a gate of type  $i$  = input cap/cap of inverter  
 $h_i$  = fanout of gates of type  $i$  = load cap/input cap

Logical Effort B

CMOS VLSI Design

Slide 24

## Question

- ❑ If delay thru one gate is  $p + hg$ ,
  
- ❑ Can we simplify multistage to something like  $P+HG$ ?

Logical Effort B

CMOS VLSI Design

Slide 25

## Overall Delay

- ❑ delay thru circuit =  $\sum \text{delay}(i)$ 
  - where  $\text{delay}(i)$  = delay thru  $i$ 'th “stage” of logic
- ❑  $\text{delay}(i) = p_i + h_i * g_i$ 
  - $p_i$  function only of gate type at stage  $i$
  - $g_i$  function only of gate type at stage  $i$ 
    - input cap/cap of inverter
  - $h_i$  depends on connected gates at stage  $i+1$ 
    - total load on output of gate  $i$ /input cap of gate  $i$
- ❑ **Thus delay =  $\sum(p_i + h_i * g_i) = \sum(p_i) + \sum(h_i * g_i)$**
- ❑ Clearly  $P = \sum(p_i)$
- ❑ *Can we write  $\sum(h_i * g_i)$  as some  $H*G$ ?*

Logical Effort B

CMOS VLSI Design

Slide 26


(p. 164)

## Definitions

□ **Path Logical Effort**  $G = \prod g_i$

□ **Path Electrical Effort**  $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 □ **Path Effort**  $F = \prod f_i = \prod g_i h_i$



Question: Can we write  $F = GH$ ?

Logical Effort B

CMOS VLSI Design

Slide 27

## Can We State $F = GH$ ?

- **No!** Consider paths that **branch**:
- Not all load at one stage is on path to output

- Individual terms

$g_1 = g_2 = 1$  (inverters)

$h_1 = (15 + 15) / 5 = 6$

$h_2 = 90 / 15 = 6$

- Path Terms


$G = \prod g_i = 1 \times 1 = 1$

$H = C_{\text{out}} / C_{\text{in}} = 90 / 5 = 18$

Thus  $GH = 18$

Versus  $F = g_1 h_1 g_2 h_2 = 36 = 2GH \neq GH$

Branch point

 

Question: What did GH overlook?

Logical Effort B

CMOS VLSI Design

Slide 28

# Branching Effort

- Introduce **Branching Effort B**
  - Accounts for signal branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i \qquad \prod h_i = BH$$

- Now we compute the **Path Effort F = GBH**
- Or **delay = P + GBH**


Logical Effort B

CMOS VLSI Design

Slide 29
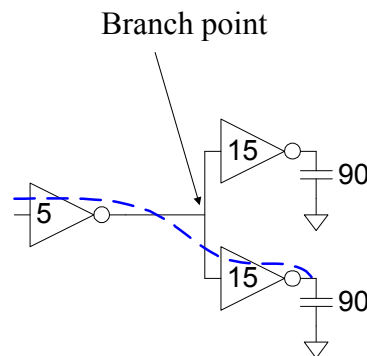
# Redo

- Individual terms
  - $g_1 = g_2 = 1$  (inverters)
  - $h_1 = (15 + 15) / 5 = 6$
  - $h_2 = 90 / 15 = 6$
  - $b_1 = (15 + 15) / 5 = 2$
  - $b_2 = 90 / 90 = 1$
- Path Terms
  - $G = \prod g_i = 1 \times 1 = 1$
  - $H = C_{\text{out}} / C_{\text{in}} = 90 / 5 = 18$
  - $B = 2 \times 1 = 2$
  - Thus  $GBH = 36$
  - Versus  $F = g_1 h_1 g_2 h_2 = 36!$



**In this case:  
exact match**

Logical Effort B

CMOS VLSI Design

Slide 30

# Designing Fast Multistage Circuits

Logical Effort B

CMOS VLSI Design

Slide 31

## Designing Fast Circuits

$$D = \sum d_i = D_F + P = \sum f_i + \sum p_i = P + F = P + GBH$$

- D is **Path Delay**
- P is **Path Parasitic Delay** - independent of widths
- F is **Path Effort**
  - $G = \prod g_i =$  **Path Logical Effort** – ind. of width
  - B = **Branching Factor**
  - $H = C_{\text{outpath}}/C_{\text{inpath}} =$  **Path Electrical Effort**

- To minimize  $\sum f_i$  when GBH is constant:
  - **MAKE EACH STAGE HAVE SAME EFFORT  $f^\wedge$**
  - For N stage circuit:  $f^\wedge = (GBH)^{1/N}$

- **Minimum possible delay =  $P + Nf^\wedge$ !!!!**

Logical Effort B

CMOS VLSI Design

Slide 32



# How Do We Find Gate Sizes to Reach this Equal Effort?

- ❑ How wide should gates be for least delay?
- ❑ Typically  $C_{in}$  of first gate is pre-specified
- ❑ Working backward from load,
  - apply transformation to find input capacitance of each gate, given the load it drives.
  - Use this for the load capacitance on previous stage
- ❑ Check work by verifying input cap spec i
- ❑ Then use input cap of each gate to size each gate

$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


Logical Effort C

CMOS VLSI Design

Slide 33
 
## Example: 3-stage path

- ❑ Select input capacitance x and y for least delay from A to B, given capacitance on A is 8C




- Input cap speced at 8C:
- Min size NAND gives  $C_{in} = 4C$
  - Thus scale widths 2X
  - or n-type are  $2 \times 2 = 4$  wide
  - p-type are also  $2 \times 2 = 4$  wide

Logical Effort C

CMOS VLSI Design

Slide 34

## Compute $f^{\wedge}$ & Delay

 


Logical Effort	$G =$
Electrical Effort	$H =$
Branching Effort	$B =$
Path Effort	$F =$
Best Stage Effort	$\hat{f} =$
Parasitic Delay	$P =$
Delay	$D =$

Logical Effort C

CMOS VLSI Design

Slide 35

## Compute $f^{\wedge}$ & Delay

 

Logical Effort	$G = (4/3) * (5/3) * (5/3) = 100/27$
Electrical Effort	$H = 45/8$
Branching Effort	$B = 3 * 2 = 6$
Path Effort	$F = GBH = 125$
Best Stage Effort	$\hat{f} = 125^{1/3} = 5$
Parasitic Delay	$P = 2 + 3 + 2 = 7$
Delay	$D = N\hat{f} + P$ $= 3*5 + 7 = 22$

*slope*

Logical Effort C

CMOS VLSI Design


Slide 36

# Work Backwards

□ Work backward for sizes using  $C_{in[i]} = C_{out[i]} \cdot g_i / f^{\wedge}$

y =

x =

 

Logical Effort C


CMOS VLSI Design

Slide 37

# Work Backwards

□ Work backward for sizes using  $C_{in[i]} = C_{out[i]} \cdot g_i / f^{\wedge}$

y =  $45 \cdot (5/3) / 5 = 15$

 

Logical Effort C

CMOS VLSI Design


Slide 38

# Work Backwards

- Work backward for sizes using  $C_{in[i]} = C_{out[i]} \cdot g_i / f^{\wedge}$

$$y = 45 \cdot (5/3) / 5 = 15$$
 
$$x = (15 \cdot 2) \cdot (5/3) / 5 = 10$$



Logical Effort C

CMOS VLSI Design

Slide 39


# Work Backwards

- Work backward for sizes using  $C_{in[i]} = C_{out[i]} \cdot g_i / f^{\wedge}$

$$y = 45 \cdot (5/3) / 5 = 15$$

$$x = (15 \cdot 2) \cdot (5/3) / 5 = 10$$
 
$$A = (10 + 10 + 10) \cdot (4/3) / 5 = 8 \text{ AND IT CHECKS!}$$




Logical Effort C

CMOS VLSI Design

Slide 40
 
## Size Last Gate

- Now size last stage:  $x = 15$ 
  - 2 input NOR has unit input cap of 5
  - To get an input cap of 15  $\Rightarrow$  widths  $15/5 = 3X$  unit!
  - $\Rightarrow$  p-type are  $3*4 = 12$  wide
  - $\Rightarrow$  n-type are  $3*1 = 3$  wide




Logical Effort C

CMOS VLSI Design

Slide 41
 
## Size Middle Gate

- Now size 2<sup>nd</sup> stage 3 input NAND
  - $y = 10$ ;
  - unit input cap of 5  $\Rightarrow$  widths  $10/5 = 2X$  unit!
  - p:n ratio of 2:3  $\Rightarrow$  p-type are  $2*2 = 4$  wide
  - $\Rightarrow$  n-type are  $3*2 = 6$  wide




Logical Effort C

CMOS VLSI Design

Slide 42
 
## Size First Gate

- Now size 1st stage
  - Cin = 8; 2 input NAND has
    - unit input cap of 4 => widths 8/4 = 2X unit!
    - p:n ratio of 1:1 => p-type are 2\*2 = 4 wide  
=> n-type are 2\*2 = 4 wide




Logical Effort C

CMOS VLSI Design

Slide 43
 
## Checking Delay

- Let's check delay
  - $d_1 = g_1 h_1 + p_1 = \{(10+10+10)/8\} * (4/3) + 2 = 7$
  - $d_2 = g_2 h_2 + p_2 = \{(15+15)/10\} * (5/3) + 3 = 8$
  - $d_3 = g_3 h_3 + p_3 = \{45/15\} * (5/3) + 2 = 7$
  - delay = 7 + 8 + 7 = 22
  - in 65nm process  $\tau = 3ps$ , so circuit is  $22 * 3 = 66ps$




Logical Effort C

CMOS VLSI Design

Slide 44
 
## What If We Try to Tweak?

- What if we made stage 2 even bigger (to be faster)
  - $d_2 = g_2 h_2 + p_2 = \{(15+15)/15\} * (5/3) + 3 = 6.3$  (*faster*)
  - but  $d_1 = g_1 h_1 + p_1 = \{(15+15+15)/8\} * (4/3) + 2 = 9.5$  (*slower*)
  - and  $d_3 = g_3 h_3 + p_3 = \{45/15\} * (5/3) + 2 = 7$  (no change)
  - delay =  $9.5 + 6.3 + 7 = 22.8 > 22$  – **SLOWER CIRCUIT**



Logical Effort C

CMOS VLSI Design

Slide 45

## Choosing Best # of Stages

- Many logic functions have multiple possible circuits (**topologies**)
- Goal: select topology, est. delay, & size transistors
- We know in general
  - NANDs better than NORs
  - Gates with fewer inputs better than more inputs
- **Typical shortcut: estimate delay by # of stages**
  - Assuming constant “gate delay”
  - and thus shorter paths are faster
- **THIS IS NOT ALWAYS TRUE!**
  - *Eg: Adding inverters at end with increasing sizes can speed up circuit, esp. when high load*


Logical Effort C

CMOS VLSI Design

Slide 46
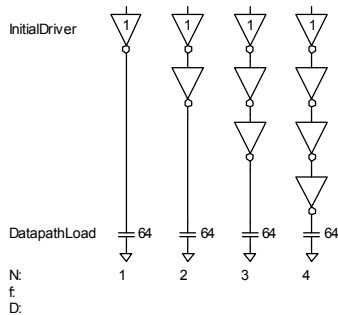
## Example (p. 166)

- ❑ How many stages should a path use?
  - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter
  - Each bit eqvt to unit inverter in load



Logical Effort C

CMOS VLSI Design

Slide 47

## Best Number of Stages

- ❑ How many stages should a path use?
  - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter


$$H = 64$$

$$G = 1$$

$$F = HG = 64$$

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

 

Logical Effort C

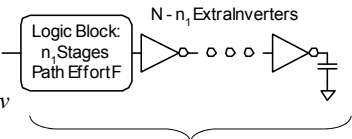
CMOS VLSI Design

Slide 48



# General Derivation

- Consider **adding inverters** to end of  $n_1$  stage path
  - How many give least delay?

$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$


The diagram shows a logic block labeled 'Logic Block: n<sub>1</sub> Stages Path Effort F' connected to a series of  $N - n_1$  inverters. The inverters are represented by a sequence of circles with a triangle pointing down, connected by a line. The final inverter is connected to ground.

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

N total stages with  $(N - n_1)$  Inverters

- do not change logical effort
- do add parasitic delay

- Define **best stage effort**  $\rho = F^{\frac{1}{N}}$


$$p_{inv} + \rho(1 - \ln \rho) = 0$$

# Best Stage Effort

- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed-form solution
- Neglecting parasitics ( $p_{inv} = 0$ ), we find  $\rho = 2.718$  (e)
- For  $p_{inv} = 1$ , solve numerically for  $\rho = 3.59$
- Again,
  - these  $\rho$  values are best logical effort per stage
  - when you have  $\hat{N} = \log_{\rho} F$  stages
 
# Sensitivity Analysis

- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - We can be sloppy!
  - Book likes  $\rho = 4$**


Logical Effort C

CMOS VLSI Design

Slide 51
 
# 1<sup>st</sup> Example, Revisited

- Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.



- Decoder specifications:
  - 16 word register file
  - Each word is 32 bits wide
  - Each bit presents load of 3 unit-sized transistors
  - True and complementary address inputs A[3:0]
  - Each input may drive 10 unit-sized transistors
- Ben needs to decide:
  - How many stages to use?
  - How large should each gate be?
  - How fast can decoder operate?

Logical Effort C

CMOS VLSI Design

Slide 52

## What Does This Mean?

- ❑ 16 word register file
  - There are 16 separate row lines
  - Branching factor of 16 at end
- ❑ Each word is 32 bits wide & each bit presents load of 3 unit-sized transistors
  - The load on each row line is  $32 \times 3 = 96$
- ❑ True and complementary address inputs A[3:0]
  - Any address input needed for only 8 row lines
- ❑ Each input may drive 10 unit-sized transistors
  - Total input capacitance from 1<sup>st</sup> stage gates on inputs = 10

Logical Effort C

CMOS VLSI Design

Slide 53

## Number of Stages

- ❑ Decoder effort is mainly electrical and branching
  - Electrical Effort:  $H = (32 \times 3) / 10 = 9.6$
  - Branching Effort:  $B = 8$
- ❑ If we neglect logical effort (assume  $G = 1$ )
  - Path Effort:  $F = GBH = 76.8$
  - Number of Stages:  $N = \log_4 F = 3.1$
- ❑ Try a 3-stage design


Logical Effort C

CMOS VLSI Design

Slide 54
 
### 3 Stage Gate Sizes & Delay

Logical Effort:  $G = 1 * 6/3 * 1 = 2$   
 Path Effort:  $F = GBH = 2 * 8 * 9.6 = 154$   
 Stage Effort:  $\hat{f} = F^{1/3} = 5.36$   
 Path Delay:  $D = 3\hat{f} + 1 + 4 + 1 = 22.1$   
 Gate sizes:  $z = 96 * 1/5.36 = 18$      $y = 18 * 2/5.36 = 6.7$



Logical Effort C

CMOS VLSI Design

Slide 55

### Comparison

- Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
<b>NAND2-INV-NAND2-INV</b>	<b>4</b>	<b>16/9</b>	<b>6</b>	<b>19.7</b>
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Fastest →

Logical Effort C

CMOS VLSI Design

Slide 56

## Review of Definitions

Term	Stage	Path
number of stages	1	$N$
logical effort	$g$	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{con-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	$f$	$D_F = \sum f_i$
parasitic delay	$p$	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Logical Effort C

CMOS VLSI Design

Slide 57

## Method of Logical Effort

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

- 6) Find gate sizes

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Logical Effort C

CMOS VLSI Design

Slide 58

## Limits of Logical Effort

- ❑ Chicken and egg problem
  - Need path to compute  $G$
  - But don't know number of stages without  $G$
- ❑ Simplistic delay model
  - Neglects input rise time effects
- ❑ Interconnect
  - Iteration required in designs with wire
- ❑ Maximum speed only
  - Not minimum area/power for constrained delay

Logical Effort C

CMOS VLSI Design

Slide 59

## Summary

- ❑ Logical effort is useful for thinking of delay in circuits
  - Numeric logical effort characterizes gates
  - NANDs are faster than NORs in CMOS
  - Paths are fastest when effort delays are  $\sim 4$
  - Path delay is weakly sensitive to stages, sizes
  - But using fewer stages doesn't mean faster paths
  - Delay of path is about  $\log_4 F$  FO4 inverter delays
  - Inverters and NAND2 best for driving large caps
- ❑ Provides language for discussing fast circuits
  - But requires practice to master

Logical Effort C

CMOS VLSI Design

Slide 60