

# Introduction to CMOS VLSI Design

## Semiconductor Memory

Harris and Weste, Chapter 12

25 October 2018

J. J. Nahas and P. M. Kogge

Modified from slides by Jay Brockman 2008

[Including slides from Harris & Weste, Ed 4,

Adapted from Mary Jane Irwin and Vijay Narananan, CSE Penn State  
adaptation of Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

Semiconductor Memory

Slide 1

## Outline

- Memory features and comparisons
- Generic Memory Architecture
  - Architecture Overview
  - Row and Column Decoders
  - Redundancy and Error Correction
- Static Random Access Memory (SRAM)
- Dynamic Random Access Memory (DRAM)
- Flash (EEPROM) Memory
- Other Memory Types

Semiconductor Memory

CMOS VLSI Design

Slide 2

# Memory Features and Comparisons

Semiconductor Memory

CMOS VLSI Design

Slide 3

## Memory Characteristics

- ❑ Read/Write Attributes
  - **Read-Only Memory** (ROM): Programmed at manufacture
    - Being phased out of use in favor of Flash
  - **Read-Write Memory**: Can change value dynamically
    - SRAM, DRAM
  - **Read-Mostly**: Can write, but much more slowly than read
    - EEPROM (Electrically Erasable, Programmable Read Only Memory) (pronounced “Double E Prom”)
    - Flash (A form of EEPROM)
- ❑ Volatility: sensitivity to losing power
  - **Volatile**: loses contents when power turned off
  - **Non-volatile**: does not lose contents

Semiconductor Memory

CMOS VLSI Design

Slide 4

# Memory Characteristics

- ❑ Addressability
  - **Random-Access**: provide address to access a “word” of data
    - No correlation between successive addresses
  - **Block oriented**: read and write large blocks of data at a time
  - **Content-addressable**: search memory for match against partial data
  - **Serial Access**: e.g.. FIFO. Queue, stack
- ❑ **Wearout**
  - Some memories have a limited number of write cycles before changing characteristics renders them unusable
- ❑ **Cell Size**
  - Primary determinant of the physical size of the memory array

# Lecture Focus

- ❑ The most used technologies
  - **SRAM**
    - Local memory
    - Registers, Cache
  - **DRAM**
    - Main memory for computers and processors
  - **Flash** and other EEPROMs
    - Program and data storage
    - Operational parameter storage
      - Used in controllers for everything from a key fob to an automobile engine/transmission.

# Memory Features


|                                   | SRAM                               | DRAM        | Flash                            |
|-----------------------------------|------------------------------------|-------------|----------------------------------|
| Non-volatile                      | No                                 | No          | Yes                              |
| Cell Size (F <sup>2</sup> )       | 25 to 40                           | 6 to 8      | 4 to 5                           |
| Read Access Time                  | ~ 0.1 ns                           | ~ 10 ns     | ~ 10 ns                          |
| Write Time                        | ~ 0.1 ns                           | ~ 10 ns     | N.A.                             |
| Erase Time                        | N.A.                               | N.A.        | ~ 10 ms                          |
| Program Time                      | N.A.                               | N.A.        | ~ 10 us                          |
| Wearout                           | N.A.                               | N.A.        | 10k to 100k erase/program cycles |
| Use in Computer/Processor Systems | Registers<br>Cache<br>(L1, L2, L3) | Main Memory | Program and Data Storage         |

- ❑ Note: Flash is process compatible with SRAM but DRAM is not.

# Generic Memory Architecture

**Westre and Harris, Chapter 12**
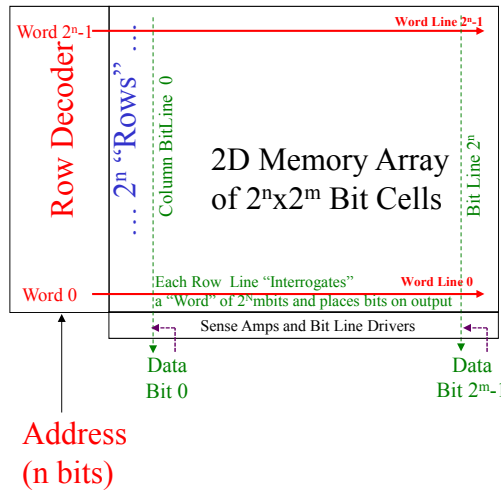
# Notional 2 Dimensional Memory ( $2^n$ Words of $2^m$ bits each)



## Architecture

- Array of  $2^n$  horizontal **word lines**
- and  $2^m$  vertical **Bit lines**
- With a "memory bit" at each intersection

## Key Logic Cells:

- **Bit Cell**: when its word line is active, place its current value on bit line
- **Row Decoder**: Convert  $2^n$  bit address into 1 out of  $2^n-1$  lines
- **Sense Amps**: convert minute signal on a bit line into full-fledged digital signal
- **Bit Line Driver**: Drives input data onto bit line for storage in cell


Semiconductor Memory

CMOS VLSI Design

Slide 9
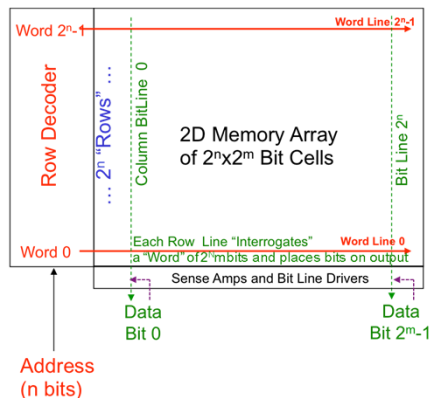
# Read Access Signal Flow

- ❑ Transmit Row Address "UP" thru row decoder
- ❑ Decoder at each row determines if it matches transmitted row address
- ❑ If so, it raises its **word line**
- ❑ As word line signal goes from left to right, each cell it reaches places its data onto its **bitline**
- ❑ Only one cell per column places its data on bit line
- ❑ Signal travels down the bit line
- ❑ When signal arrives at Sense Amp, it is amplified and converted into full digital value




Semiconductor Memory

CMOS VLSI Design

Slide 10

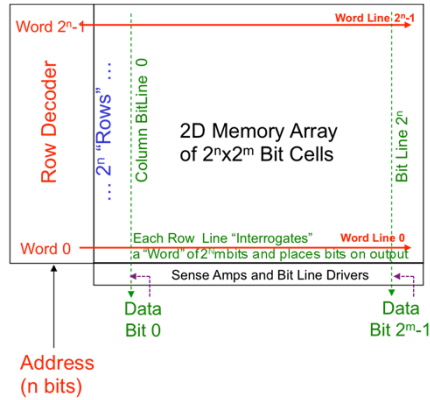
# Write Access Signal Flow

- ❑ Transmit Row Address “UP” thru row decoder
- ❑ Decoder at each row determines if it matches transmitted row address
- ❑ If so, it raises its **word line**
- ❑ As word line signal goes from left to right, each cell it reaches receives its data from its **bitline**
- ❑ Only one cell per column receives data from its bit line




# Questions

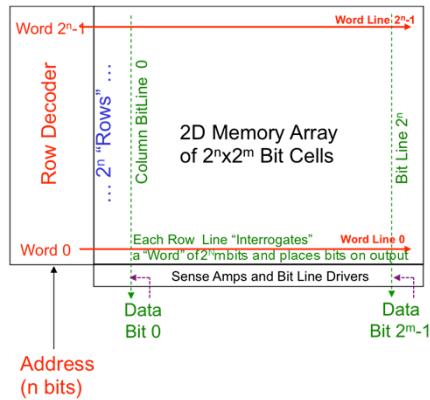1. How many bits of storage?
2. What is logic function at each row decoder?
3. What memory parameters have major effect on access time, and why?
4. What memory parameters affect power?
5. What happens if memory is “tall and skinny”? i.e.  $n \gg m$
6. What happens if memory is “short and fat”? i.e.  $n \ll m$


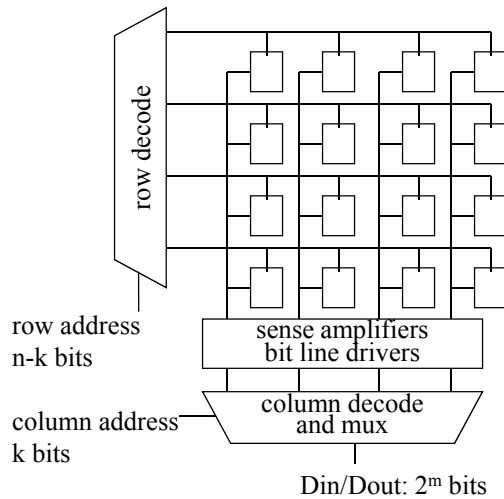
## More Accurate Array-Structured Memory Architecture

Assume we still want  $2^n$  words of  $2^m$  bits each,  
but implement 2D array of  $(2^{n-k})$  rows of  $(2^{k+m})$  bits




CMOS VLSI Design

- ❑ Address of  $n$  bits, split into two parts
  - “Row” ( $n-k$  bits)
  - “Column” ( $k$  bits)
- ❑  $n-k$  row address bits used to decode 1 of  $2^{n-k}$  rows
- ❑ All cells on selected row sensed simultaneously
- ❑ Array reads out  $(2^k) \times (2^m)$  bits – called an **open row**
- ❑  $C$  Column address bits select one of  $2^k$  words from open row
 
## What About the Bit Lines

- ❑ Each bit line has multiple ( $2^{n-k}$ ) cells on it
- ❑ Only one cell is “active” at a time
  - Remember: its “activated” by row line
- ❑ How do we drive one line from so many sources?
  - Key parameter: what is “area” per cell
    - # of transistors, size of transistors, ...
  - Do we treat column as a “wire” or as part of a circuit?
  - If so, can we simplify by placing part of circuit “at top?”
- ❑ Option 1: Tri-state drivers?
- ❑ Option 2: Multi-legged NAND?
- ❑ Option 3: Multiplexor-like pass transistors?



Semiconductor Memory

CMOS VLSI Design


Slide 14

## A Common Solution: Active Pull-up

- Use “High Resistance” P type at top
- Turn on for access
- Bit line pulled high
- Bit cell must pull down if “1” not desired value

Questions:

 1. What width transistors do we want for the bit cell pull downs?
2. Many early designs have P-type always on. Why is that bad?
3. Why is P type “high resistance”?



Semiconductor Memory

CMOS VLSI Design

Slide 15

## Dynamic Sensing

- With all P types always on, when n-types are on you have “short circuit” current – wastes power
- Observation: a bit line is a long wire
  - With significant capacitance
- What if we “pulse” p –types just before reading
  - Called **precharging** the bit lines
  - Bit lines all “charged” to a high voltage
- Now when we activate n-types
  - Only bits that represent “0” are pulled low
  - NO SHORT CIRCUIT CURRENT
- “Sensing:” no longer static voltage level
  - Charge on bit line decays with time
  - Need sampling **sense amplifier** to sense charge

Semiconductor Memory


CMOS VLSI Design

Slide 16




# Row and Column Decoders
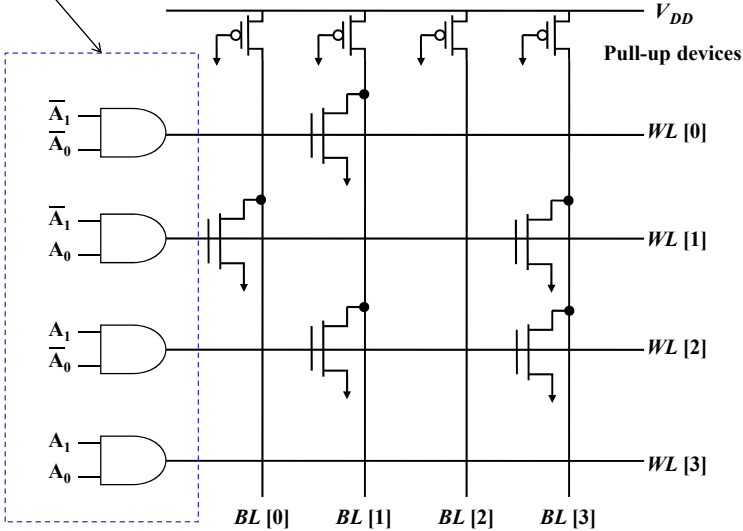
## Row Decoder: n bit address in, 2<sup>n</sup> rows out



# Standardizing Row Decoder

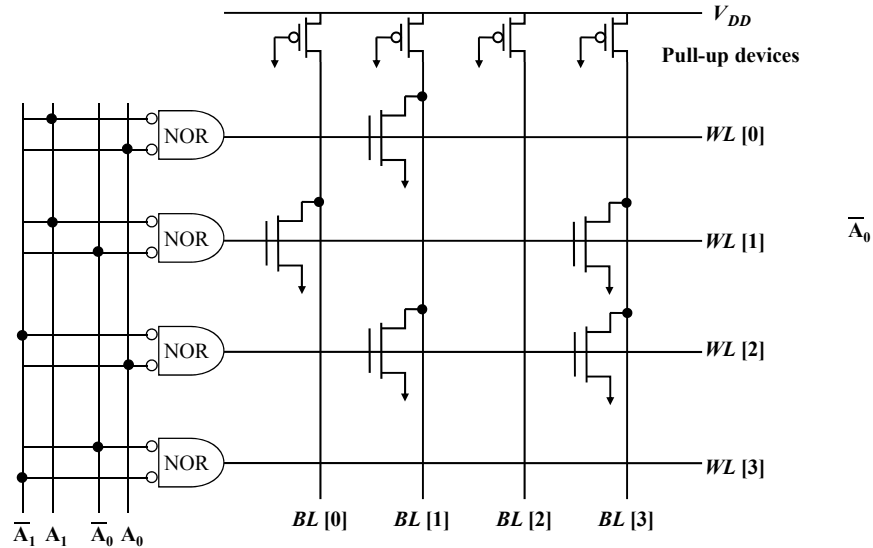

# Row Decoders

Collection of  $2^n$  complex logic gates  
 Organized in regular and dense fashion

## (N)AND Decoder

$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \bar{A}_4 \bar{A}_5 \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$


## NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{\bar{A}_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$
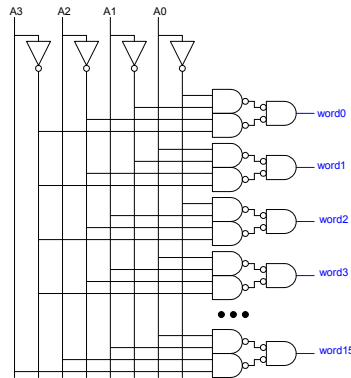
# Large Decoders

- For  $n > 4$ , NAND gates become slow
  - Break large gates into multiple smaller gates




Semiconductor Memory

CMOS VLSI Design

Slide 21
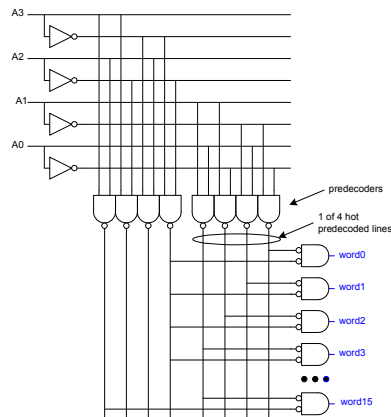
# Predecoding

- Many of these gates are redundant
  - Factor out common gates into predecoder
  - Saves area
  - Same path effort




Semiconductor Memory

CMOS VLSI Design

Slide 22
 
## 4-input pass-transistor based column decoder/multiplexor



**Advantages:** speed ( $t_{pd}$  does not add to overall memory access time)  
**Only one extra transistor in signal path**  
**Disadvantage:** Large transistor count

Semiconductor Memory

CMOS VLSI Design

Slide 23

## Redundancy and Error Correction

**Weste and Harris Section 12.8 and 11.7.2**

Semiconductor Memory

CMOS VLSI Design

Slide 24

# Redundancy

- ❑ To improve yield, large memory arrays typically have redundant rows and columns.
- ❑ During testing, defective bits, rows, and columns are identified.
- ❑ Algorithm then determines which rows and/or columns to replace to avoid the defective bits.
- ❑ Laser programming or fuses are used to program the replacements into the chip

# Error Correction

- ❑ Large memory arrays can also have soft errors due to signals being marginal.
  - The larger the number of bits, the larger the distribution of signals.
  - What is the error rate for a memory?
    - 1 error in  $10^{12}$  reads is not acceptable
    - 1 error in  $10^{16}$  reads is acceptable for most applications
      - A few errors per year at 1 GHz read rate.
    - 1 error in  $10^{24}$  reads is needed for applications in financial institutions
- ❑ A 64 bit word plus nine parity bits (73 bits total) can be used to correct one bit error in the 64 bit word and detect two bit errors.
  - The use of 64 bit single error correction would decrease the error rate from 1 error in  $10^{12}$  to 1 error in  $10^{16}$  reads.

# SRAM: Static Random Access Memory


Weste and Harris  
Section 12.2

Semiconductor Memory

CMOS VLSI Design

Slide 27

## Intel Nehalem I7 Processor

 

- ❑ 2008, 45 nm CMOS
- ❑ SRAM used in registers, L1 and L2 Caches in Cores and Shared L3 Cache
- ❑ 90+% of chip is SRAM


Semiconductor Memory

CMOS VLSI Design

Slide 28
 
# Commercial SRAMs

- Five generations of Intel SRAM cell micrographs
  - Transition to thin cell at 65 nm
  - Steady scaling of cell area




Semiconductor Memory

CMOS VLSI Design

Slide 29

## 6-transistor CMOS SRAM Cell

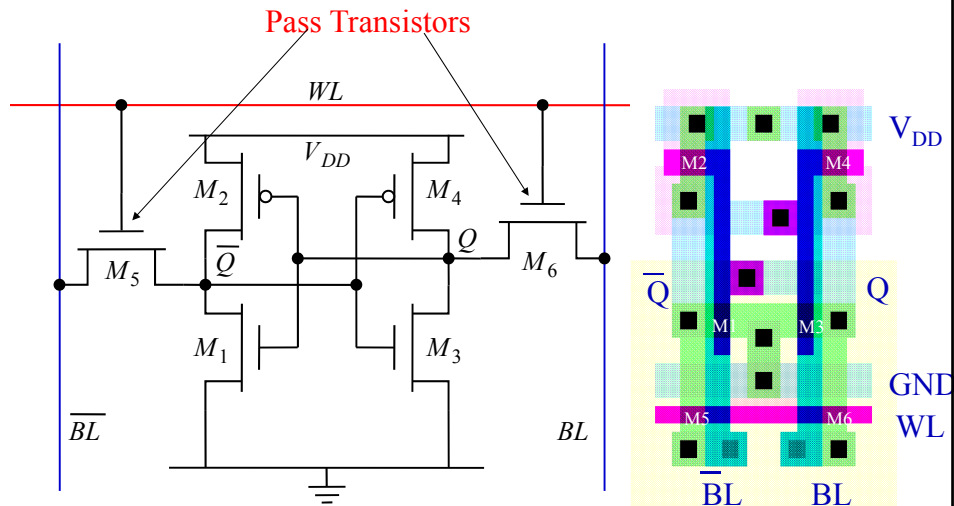

There are **2 bit lines** per column: **True** and **Complement**  
Sense Amp looks for “1-0” or “0-1”



Semiconductor Memory

CMOS VLSI Design

Slide 30
  
# SRAM Read

- ❑ Precharge both bitlines high
- ❑ Then turn on wordline
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex:  $A = 0, A_b = 1$ 
  - bit discharges, bit\_b stays high
  - But A bumps up slightly
- ❑ *Read stability*
  - A must not flip
  - $N1 \gg N2$





Semiconductor Memory

CMOS VLSI Design

Slide 31
  
# SRAM Write

- ❑ Drive one bitline high, the other low
- ❑ Then turn on wordline
- ❑ Bitlines overpower cell with new value
- ❑ Ex:  $A = 0, A_b = 1, \text{bit} = 1, \text{bit}_b = 0$ 
  - Force  $A_b$  low, then A rises high
- ❑ *Writability*
  - Must overpower feedback inverter
  - $N2 \gg P1$



Semiconductor Memory


CMOS VLSI Design

Slide 32


 
# SRAM Sizing

- ❑ High bitlines must not overpower inverters during reads
- ❑ But low bitlines must write new value into cell




Semiconductor Memory

CMOS VLSI Design

Slide 33

# SRAM Column Example

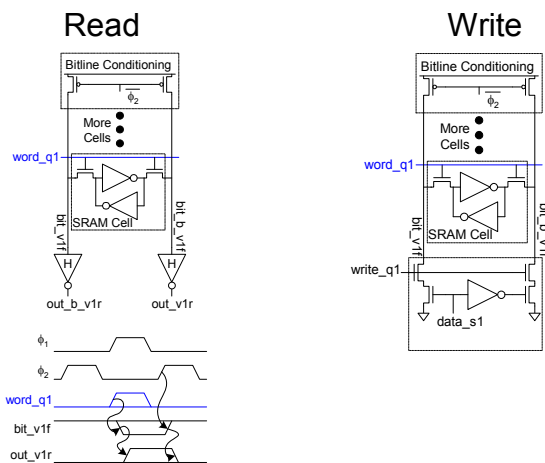


Semiconductor Memory

CMOS VLSI Design

Slide 34
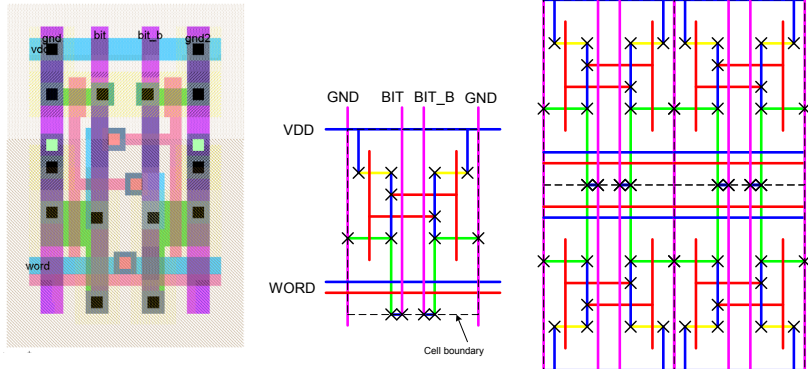
# SRAM Layout

- ❑ Cell size is critical:  $26 \times 45 \lambda$  (even smaller in industry)
- ❑ Tile cells sharing  $V_{DD}$ , GND, bitline contacts




Semiconductor Memory

CMOS VLSI Design

Slide 35
 
# Thin Cell

- ❑ In nanometer CMOS
  - Avoid bends in polysilicon and diffusion
  - Orient all transistors in one direction
- ❑ *Lithographically friendly or thin cell layout* fixes this
  - Also reduces length and capacitance of bitlines




Semiconductor Memory

CMOS VLSI Design


Slide 36

## Bitline Conditioning

- ❑ Precharge bitlines high before reads

 

 - ❑ Equalize bitlines to minimize voltage difference when using sense amplifiers




## Sense Amplifiers

- ❑ Bitlines have many cells attached
  - Ex: 32-kbit SRAM has 128 rows x 256 cols
  - 128 cells on each bitline
- ❑  $t_{pd} \propto (C/I) \Delta V$ 
  - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - Discharged slowly through small transistors (small I)
- ❑ *Sense amplifiers* are triggered on small voltage swing (reduce  $\Delta V$ )


 
# Decoder Layout

- ❑ Decoders must be pitch-matched to SRAM cell
  - Requires very skinny gates





**Pre-decoders help reduce size of decoders.**

# Dynamic RAM (DRAM)

Weste and Harris  
Section 12.3

## Intel 1103 1Kbit 1024 x 1 DRAM

  

[http://www.cpu-museum.com/Thumbs/Intel-P1103\\_t.jpg](http://www.cpu-museum.com/Thumbs/Intel-P1103_t.jpg)

- Four arrays of 256 bits
- Each array is 16 X 16
- 4 cell symmetry
- On-pitch word line driver and sense amplifiers.

- ❑ First commercial DRAM. Introduced in 1970
- ❑ Replaced core memory on mainframe computers


[http://cdn.dipity.com/uploads/events/8d74b8890633acbbdf01e3508c7bfe0\\_1M.png](http://cdn.dipity.com/uploads/events/8d74b8890633acbbdf01e3508c7bfe0_1M.png)

Semiconductor Memory


CMOS VLSI Design

Slide 43

## Some More Modern DRAMs

 


256Mb DRAM

 


2008 DDR3 DRAM

 [http://www.cetasia.com/IMAGES/EEOL\\_2008APR24\\_STOR\\_NP\\_01a.jpg](http://www.cetasia.com/IMAGES/EEOL_2008APR24_STOR_NP_01a.jpg)



42 nm 2Gb DRAM die
 
<http://legitreviews.com/images/news/2010/42-nm-DRAM-die.jpg>



Prototype 1/2 Gb DRAM for 3D Stacks


<http://eda360insider.files.wordpress.com/2011/08/micron-hmc-memory-die-photo.jpg?w=571&h=442>

Semiconductor Memory

CMOS VLSI Design

Slide 44

# 1-Transistor DRAM Cell

 



- $C_s$  stores either a charge or no charge (“1” or “0”)
- When word line active, transistor connects cap to bit line
- Charge on  $C_s$  distributed onto bit line
- This changes voltage on bit line

Semiconductor Memory

CMOS VLSI Design

Slide 45

# DRAM Operation

  

Write:  $C_s$  is charged or discharged by asserting WL and BL.

Read: First precharge BL to  $V_{DD}/2$

During Read, charge redistribution takes places between  $C_{BL}$  &  $C_s$

Sense difference in voltage from  $V_{DD}/2$

If  $C_s$  “charged” to  $>V_{DD}/2$ , BL pulled “up” a bit

If  $C_s$  discharged, BL pulled “down” a bit

$$\Delta V \text{ proportional to } C_s / (C_s + C_{BL})$$

Ratio tends to be static across multiple generations


Voltage swing is small; typically around 250 mV.

Semiconductor Memory

CMOS VLSI Design

Slide 46
 
# Early Poly Diffused Capacitor DRAM Cell



**Cross-section**

**Layout**


Uses Polysilicon-Diffusion Capacitance  
Expensive in Area

Semiconductor Memory

CMOS VLSI Design

Slide 47
 
## SEM of poly-diffusion capacitor 1T-DRAM




Semiconductor Memory

CMOS VLSI Design

Slide 48



# Capacitor Implementations

 


[http://www.ieee.org/portal/cms\\_docs\\_sscs/sscs/08Winter/sunami-fig5.jpg](http://www.ieee.org/portal/cms_docs_sscs/sscs/08Winter/sunami-fig5.jpg)

Semiconductor Memory

CMOS VLSI Design

Slide 49

# Trench Capacitor (Fig. 12.42)

 


Semiconductor Memory


CMOS VLSI Design

Slide 50

# Making the DRAM Capacitors

 

Trench Cell

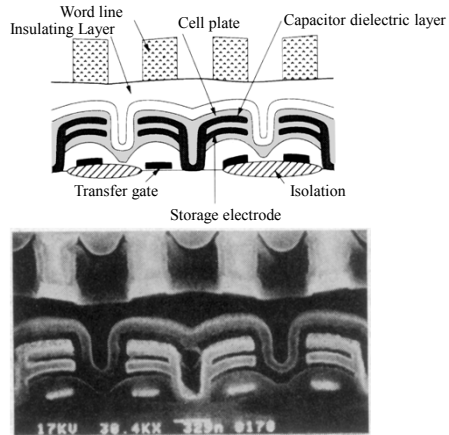

Stacked-capacitor Cell

Semiconductor Memory

CMOS VLSI Design

Slide 51

# DRAM Folded Bitline Subarray

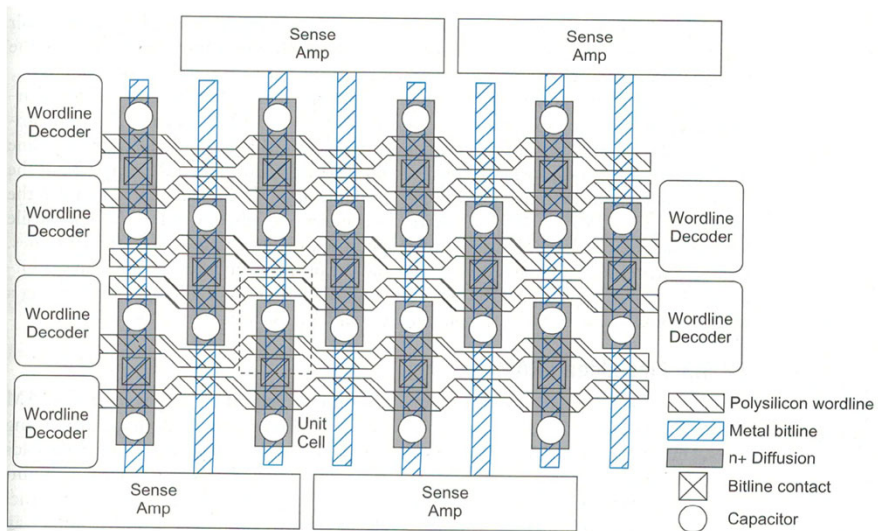


FIGURE 12.46 Layout of folded bitline subarray

Semiconductor Memory

CMOS VLSI Design

Slide 52

# DRAM Sense Amplifier

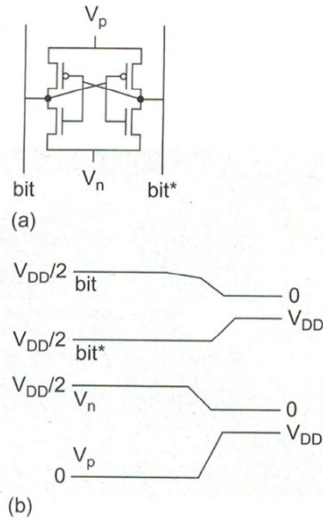


FIGURE 12.47 Sense amplifier

Semiconductor Memory

CMOS VLSI Design

Slide 53

# DRAM Refresh

- ❑ Memory capacitor can discharge by themselves in  $\sim 10$ -100 ms.
- ❑ A read operation senses the capacitor voltage and, using positive feedback, recharges the capacitor.
- ❑ All bit cells in a DRAM must be read periodically to refresh the capacitor voltage.
  - This periodic reading is called a refresh cycle.

Semiconductor Memory

CMOS VLSI Design

Slide 54

# Flash Memory


Weste and Harris  
Section 12.4.3

Semiconductor Memory


CMOS VLSI Design

Slide 55
 
## Non-Volatile Memories The Floating-gate transistor (FAMOS)



Device cross-section

 

Schematic symbol



- Storage determined by charge on the floating gate
  - "0" = negative charge (extra electrons)
  - "1" = no charge
- Negative charge on floating gate "screens" normal gate, raising threshold
- Charge can take years to "leak off" once placed there
- Multi Level** flash: different charge levels represent different values
  - We are "programming"  $V_t$  of the transistor

Semiconductor Memory

CMOS VLSI Design

Slide 56

# NAND Flash Memory "String"

  

- All wordlines other than the one to be read are  $\gg$  "0" threshold, so they turn on.
- Wordline to be read has lower voltage:
  - If cell has "0" – no current
  - If cell has "1" – device is on

Picture courtesy of Toshiba

Semiconductor Memory

CMOS VLSI Design

Slide 57

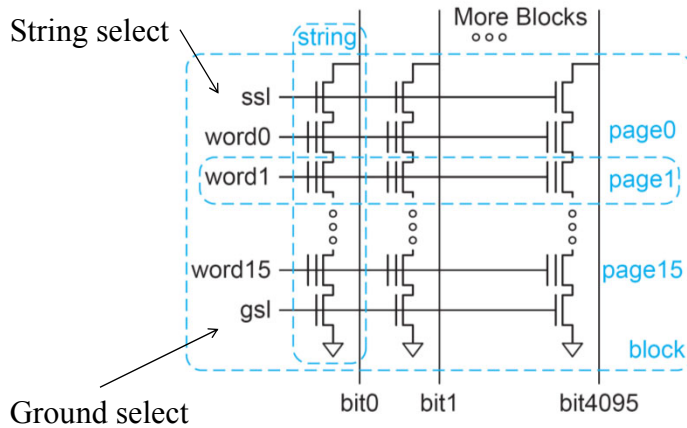
 


FIGURE 12.60 NAND Flash string

Semiconductor Memory

CMOS VLSI Design

Slide 58

# NAND Flash Memory

The diagram illustrates the NAND Flash Memory structure. It shows a grid of memory cells. The horizontal lines are labeled "Word lines" and the vertical lines are labeled "Bit line contact" and "Source line contact". The cells are connected to these lines through "Select transistors". The "Active area" is indicated by a horizontal arrow, and "STI" (Shallow Trench Isolation) is shown between the cells. A photograph of a 64 Gb (8GB) flash chip is shown on the right, with labels for "Sense Amp", "Row Decoder", "32 Gb Plane 0", "32 Gb Plane 1", and "Sense Amp Peripheral Circuits".


- 64 Gb (8GB) flash
- 2 independent panes
- 64K columns/pane
- Thus 64kbit page
- Each cell holds 4 bits
- Each string = 64 cells
- Each block has 256 pages
- Each pane has 2K blocks

Courtesy Toshiba

Semiconductor Memory CMOS VLSI Design Slide 59
 
## Reading Data

- Precharge bit lines
- SSL & GSL set high
- Set **all word lines but** desired page to high enough to turn transistors on, regardless of state
- Set **word line for desired page** high enough to turn on IF NO CHARGE ("1") is present on floating gate
- Result depends on floating gate:
  - If no charge (1), all transistors on & bit line discharged
  - If negatively charged (0), bit line charge not disturbed



Question: Why do we have *string select* and *ground select* transistors?



Semiconductor Memory

CMOS VLSI Design

Slide 60


  
## Non-Volatile Memories The Floating-gate transistor (FAMOS)



- **ERASE:** Raising substrate to high + voltage (e.g. 20V) with Gate at Ground, causes tunneling from floating gate to substrate, clearing floating gate of all charge
- **PROGRAM:** High + voltage on Control Gate, with substrate at ground, causes electrons to tunnel from substrate to floating gate, raising effective threshold of device, and representing a "0"
  - Different voltages can store different amounts of charge, changing threshold
- **READ** state by applying voltage (< "0" threshold) to control gate and seeing if current flows


|       |               |           |                |                 |
|-------|---------------|-----------|----------------|-----------------|
| 0 V   | 20 V          | 20 V      | 20 V           | 10 V            |
|       |               |           |                |                 |
| 20 V  | 20 V          | 0 V       | 0 V            | 0 V             |
| Erase | Inhibit Erase | Program 0 | Do Not Program | Inhibit Program |

Semiconductor Memory

CMOS VLSI Design

Slide 63

## Summary

 

|       |               |           |                |                 |
|-------|---------------|-----------|----------------|-----------------|
| 0 V   | 20 V          | 20 V      | 20 V           | 10 V            |
|       |               |           |                |                 |
| 20 V  | 20 V          | 0 V       | 0 V            | 0 V             |
| Erase | Inhibit Erase | Program 0 | Do Not Program | Inhibit Program |

Semiconductor Memory

CMOS VLSI Design

Slide 64



# Microcontrollers


- ❑ An example of SRAM combined with Flash Memory
- ❑ Usually include many other functions

Semiconductor Memory

CMOS VLSI Design

Slide 65

# STM ARM Cortex-M3 MCU

 


Semiconductor Memory

CMOS VLSI Design

Slide 66

# STM ARM Cortex-M3 MCU

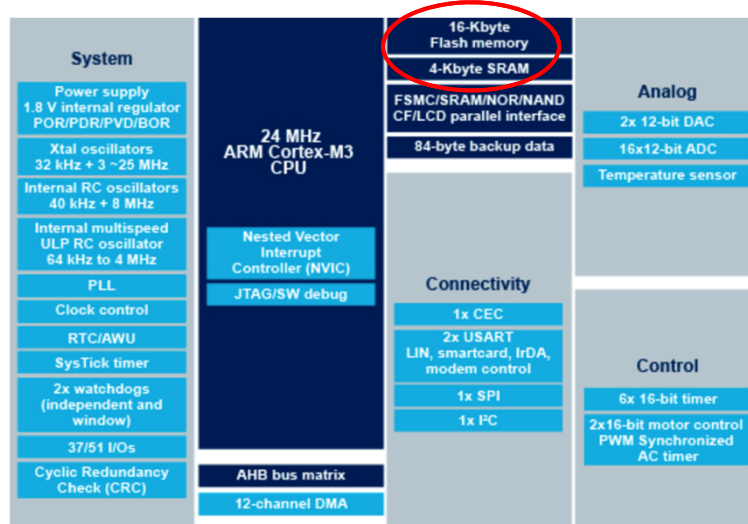

Semiconductor Memory

CMOS VLSI Design

Slide 67

# STM ARM Cortex MCUs

- Clock speed up to 400 MHz
- Flash memory up to 3 MB
- SRAM up to 1 MB

Semiconductor Memory

CMOS VLSI Design

Slide 68

# Other Semiconductor Memory Technologies


Semiconductor Memory

CMOS VLSI Design

Slide 69
 
## First Commercial MRAM

- ▶ 4 Mb Toggle MRAM
  - 35ns symmetrical read/write
  - Unlimited endurance
  - Data retention  $\gg 10$  Years
  - 256Kx16bit organization
  - 3.3V single power supply
  - Fast SRAM pinout
  - Consumer temperature range



Developed by Motorola and Freescale Semiconductor  
Spun-off as Everspin Technologies, Chandler, AZ

Joe Nahas 28 Feb 2007

CMOS VLSI Design  
Slide 70


# MRAM Attributes

- ❑ Non-Volatility
  - fast writing
  - no write endurance limitation
- ❑ Random Access
  - no refresh
  - no erase/program write sequence.
- ❑ Non-destructive read

Joe Nahas 28 Feb 2007

CMOS VLSI Design  
Slide 71

# Toggle MRAM Bit Cell

 


CMOS VLSI Design

Joe Nahas 28 Feb 2007  
Slide 72
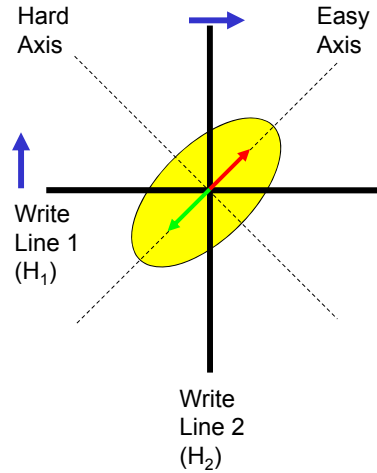
# Elements of Toggle Bit


- ❑ Balanced SAF free-layer
- ❑ Bit oriented 45° to lines
- ❑ Unipolar currents
- ❑ Overlapping pulse sequence
- ❑ Pre-read / decision write



Joe Nahas 28 Feb 2007

CMOS VLSI Design  
Slide 73


# Toggle MRAM Switching Sequence

 

Joe Nahas 28 Feb 2007

CMOS VLSI Design  
Slide 74


# 2 X 2 Array Addressing

 

Joe Nahas 28 Feb 2007

CMOS VLSI Design  
Slide 75

# Toggle MRAM Block Diagram

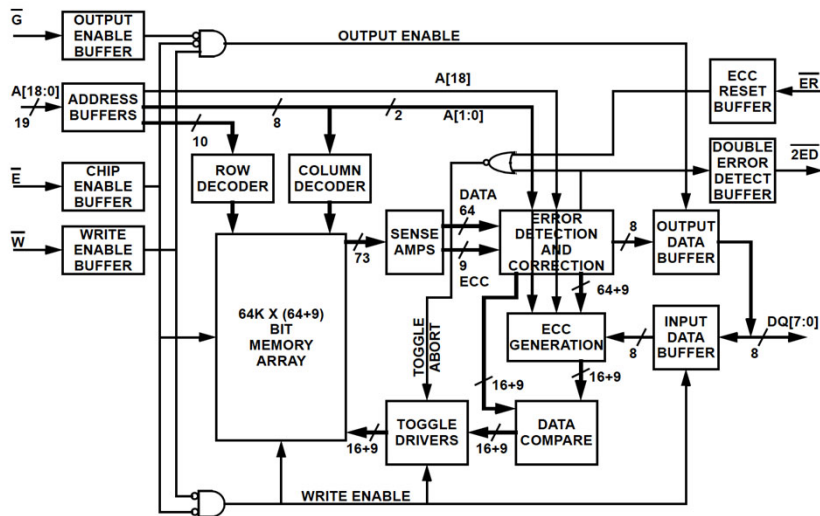


Sold by Everspin Technologies, Chandler, AZ

Semiconductor Memory

CMOS VLSI Design

Slide 76

## The Radical Fringe: Carbon Nanotubes

 

ARRAYS of carbon nanotubes, called fabrics, constitute the 0 and 1 switching elements for an innovative memory chip designed by Nantero, a section of which is shown here.


Scientific American,  
Feb. 2005

Semiconductor Memory

CMOS VLSI Design

Slide 77

## The Radical Fringe: Carbon Nanotubes

 

SAGGING AND STRAIGHTENING represent the 1 and 0 states for a random-access memory made up of groupings of nanotubes. In its 0 state, the fabric remains suspended above the electrode (*left*).

When a transistor turns on, the electrode produces an electric field that causes a nanotube fabric to bend and touch an electrode, a configuration that denotes a 1 state (*right*).

Developed by Nantera, being commercialized by LSI Logic

Semiconductor Memory

CMOS VLSI Design

Slide 78