

Introduction to CMOS VLSI Design

Quick Verilog

Lecture by Peter Kogge
Fall 2009, 2011, 2012, 2015, 2018
University of Notre Dame
Using some slides by Jay Brockman Notre Dame 2008,
and David Harris, Harvey Mudd College
<http://www.cmosvlsi.com/coursematerials.html>

Verilog

CMOS VLSI Design

Slide 1

Levels of Design Modeling

- ❑ **Structural**: how a module is “wired together” from simpler modules
 - modules defined in terms of input and output **ports**
 - “Calling” a module creates a new instance
 - With “arguments” that are named wires.
- ❑ **Behavioral**: how outputs change as function of inputs
 - Key statement type: **assignment**
 - **Continuous** assignment – for driving a wire
 - **Always** assignment – for driving a latch
- ❑ **Physical**: layout of devices on chip
- ❑ **Netlist**: list of all ports connected to each wire

Verilog

CMOS VLSI Design

Slide 2

Verilog

- ❑ **Verilog**: one of two popular **Hardware Description Languages (HDL)**
 - VHDL is the other
- ❑ Naturally modular:
 - Define new module type in terms of simpler types
 - When used, creates a new “**instance**” of module
 - With wire names between “**ports**” of instance
- ❑ Suitable for all levels of models:
 - **Behavioral**: with no other resources needed
 - **Structural**: with library of technology-specific modules
 - **Physical**: as with structural but with “place & route” to
 - **Place** individual instances on 2D chip surface
 - **Route** wires between instance ports using chip metal

Verilog

CMOS VLSI Design

Slide 3

In Following

- ❑ Courier text = sample Verilog code
- ❑ Green courier = sample use of a keyword
- ❑ <xxx> = a general syntactic term

Verilog

CMOS VLSI Design

Slide 4

MIPS8 Overview

Verilog

CMOS VLSI Design

Slide 5

MIPS Architecture

- ❑ Example: subset of MIPS processor architecture
 - Drawn from Patterson & Hennessy
- ❑ MIPS is a 32-bit architecture with 32 registers
 - Consider 8-bit subset using 8-bit datapath
 - Only implement 8 registers (\$0 - \$7)
 - \$0 hardwired to 00000000
 - 8-bit program counter
- ❑ David Harris has developed labs to implement
 - Uses Electric CAD tools
 - Illustrate the key concepts in VLSI design

8bit MIPS

CMOS VLSI Design

Slide 6

Instruction Set

Table 1.7 MIPS instruction set (subset supported)

Instruction	Function	Encoding	op	funct
add \$1, \$2, \$3	addition: \$1 → \$2 + \$3	R	000000	100000
sub \$1, \$2, \$3	subtraction: \$1 → \$2 - \$3	R	000000	100010
and \$1, \$2, \$3	bitwise and: \$1 → \$2 and \$3	R	000000	100100
or \$1, \$2, \$3	bitwise or: \$1 → \$2 or \$3	R	000000	100101
slt \$1, \$2, \$3	set less than: \$1 → 1 if \$2 < \$3 \$1 → 0 otherwise	R	000000	101010
addi \$1, \$2, imm	add immediate: \$1 → \$2 + imm	I	001000	n/a
beq \$1, \$2, imm	branch if equal: PC → PC + imm ^a	I	000100	n/a
j destination	jump: PC_destination ^a	J	000010	n/a
lb \$1, imm(\$2)	load byte: \$1 → mem[\$2 + imm]	I	100000	n/a
sb \$1, imm(\$2)	store byte: mem[\$2 + imm] → \$1	I	110000	n/a

8bit MIPS

CMOS VLSI Design

Slide 7

Instruction Encoding

- 32-bit instruction encoding
 - Requires four cycles to fetch on 8-bit datapath

format	example	encoding												
R	add \$rd, \$ra, \$rb	<table border="1" style="display: inline-table; text-align: center;"> <tr> <td style="width: 6px;">6</td> <td style="width: 5px;">5</td> <td style="width: 5px;">5</td> <td style="width: 5px;">5</td> <td style="width: 5px;">5</td> <td style="width: 6px;">6</td> </tr> <tr> <td>0</td> <td>ra</td> <td>rb</td> <td>rd</td> <td>0</td> <td>funct</td> </tr> </table>	6	5	5	5	5	6	0	ra	rb	rd	0	funct
6	5	5	5	5	6									
0	ra	rb	rd	0	funct									
I	beq \$ra, \$rb, imm	<table border="1" style="display: inline-table; text-align: center;"> <tr> <td style="width: 6px;">6</td> <td style="width: 5px;">5</td> <td style="width: 5px;">5</td> <td style="width: 16px;">16</td> </tr> <tr> <td>op</td> <td>ra</td> <td>rb</td> <td>imm</td> </tr> </table>	6	5	5	16	op	ra	rb	imm				
6	5	5	16											
op	ra	rb	imm											
J	j dest	<table border="1" style="display: inline-table; text-align: center;"> <tr> <td style="width: 6px;">6</td> <td style="width: 26px;">26</td> </tr> <tr> <td>op</td> <td>dest</td> </tr> </table>	6	26	op	dest								
6	26													
op	dest													


8bit MIPS

CMOS VLSI Design

Slide 8

MIPS Microarchitecture

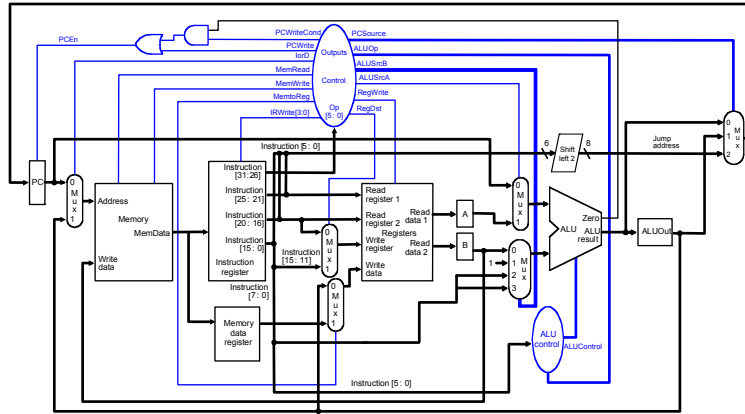- ❑ Multicycle μ architecture from Patterson & Hennessy




8bit MIPS

CMOS VLSI Design

Slide 9

Multicycle Controller

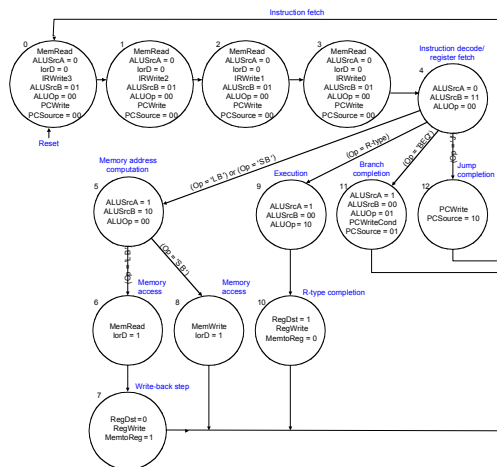


8bit MIPS

CMOS VLSI Design

Slide 10

MIPS Floorplan

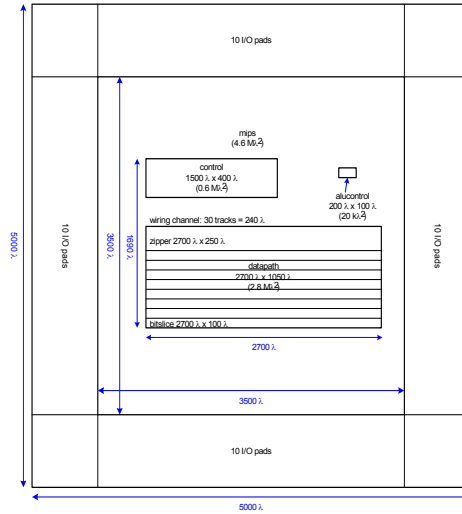


Verilog MIPS0:

CMOS VLSI Design

Slide 11

MIPS Layout

 


8bit MIPS

CMOS VLSI Design

Slide 12

Fabrication & Packaging

 - ❑ Tapeout final layout
- ❑ Fabrication
 - 6, 8, 12" wafers
 - Optimized for throughput, not latency (10 weeks!)
 - Cut into individual dice
- ❑ Packaging
 - Bond gold wires from die I/O pads to package



8bit MIPS

CMOS VLSI Design

Slide 13

Modules, Structural Design, and Netlists

Verilog

CMOS VLSI Design

Slide 14

Signal Declarations

- ❑ **wire** *<list-of-signal-names>;*
 - Each name in list is a separate net
 - Treat as an electrical “wire”
 - No “stored value”
 - echoes whatever value is currently driving it to all other terminals with no time delay
- ❑ **reg** *<list-of-signal-names>;*
 - Each name treated like a “latch”
 - “Stores” value last “assigned” to it
- ❑ **parameter** *<name> = <value>*
 - Defines a constant value as in C `const`

Verilog

CMOS VLSI Design

Slide 15

Defining Modules in Verilog

- ❑ **Module**: defines a basic circuit with some input and output signals
- ❑ **module** *<module-name>(<port-list>;*
<definitions of internal signals>;
<assignments to internal signals and output ports>;
endmodule
- ❑ *<port-list>*: list of circuit I/Os
 - Each port is a named “wire” from/to a “pad”
 - Input signals: **input** *<name>, <name>....,*
 - Output signals : **output** *<name>, <name>....,*
 - Signals that can be both: **inout** *<name>, <name>...*

Verilog

CMOS VLSI Design

Slide 16

Example

```
module carry(input a, b, c,
             output cout)
    wire x, y, z;
    and g1(x, a, b);
    and g2(y, a, c);
    and g3(z, b, c);
    or g4(cout, x, y, z);
endmodule
```

defines new module type

port description

3 internal nets

g1,...g4 instances of other module types

associating net names with ports builds internal netlist

Verilog

CMOS VLSI Design

Slide 17

Alternative Port List

```
module carry(a, b, c, cout)
    input a, b, c;
    output cout;
}
    wire x, y, z;
    and g1(x, a, b);
    and g2(y, a, c);
    and g3(z, b, c);
    or g4(cout, x, y, z);
endmodule
```

Sometimes easier to read

Verilog

CMOS VLSI Design

Slide 18

Transistor-Level Model

```


module carry(input a, b, c,
             output cout)

    wire    i1, i2, i3, i4, cn;

    tranif1 n1(i1, 0, a);
    tranif1 n2(i1, 0, b);
    tranif1 n3(cn, i1, c);
    tranif1 n4(i2, 0, b);
    tranif1 n5(cn, i2, a);
    tranif0 p1(i3, 1, a);
    tranif0 p2(i3, 1, b);
    tranif0 p3(cn, i3, c);
    tranif0 p4(i4, 1, b);
    tranif0 p5(cn, i4, a);
    tranif1 n6(cout, 0, cn);
    tranif0 p6(cout, 1, cn);
endmodule

```

tranif#(drain, source, gate)

 

Note: nets can have more than 2 tie points

Verilog

CMOS VLSI Design

Slide 19

Defining Multi-wire Signals

- ❑ Often convenient to group set of signals under same name as a **vector**
 - E.g. a data bus
- ❑ Precede name by **range specification** $[n:m]$
 - $n-m+1$ = total number of signals
 - n : “number” given to left-most signal
 - m : “number” given to right-most signal
- ❑ To access individual wire use $\langle name \rangle [i]$
- ❑ To access subset of wires use $\langle name \rangle [i:j]$
- ❑ E.g. `input [7:0] memdata` defines 8 bit bus

Verilog

CMOS VLSI Design

Slide 20

Example 4-input Ripple Adder

```
module four_bit_adder(input [3:0] a, b, input cin;
                    output [3:0] s, output cout);

    wire [3:1] c;

    fulladder fa0(a[0], b[0], cin, s[0], c[1]);
    fulladder fa1(a[1], b[1], c[1], s[1], c[2]);
    fulladder fa2(a[1], b[1], c[2], s[2], c[3]);
    fulladder fa3(a[1], b[1], c[3], s[3], cout);
endmodule;
```

Note: “order” of instance statements in code is irrelevant

Verilog

CMOS VLSI Design

Slide 21

Types of Nets in Verilog

- Wire**: a normal metal or poly line
 - driven by some single output port
 - Replicates signal at arbitrary # of input ports
- Tri**: a tri-stated wire
 - May be driven by multiple tri-stated output ports
- Supply0**: ground
- Supply1**: V_{dd}
- Wand**: wired AND
 - May be driven by multiple open collector drivers
- Wor**: wired OR
 - May be driven by multiple emitter-coupled drivers
- Triand**, **trior**: similar to above but may be three-state
- Tri0**: resistor to ground
- Tri1**: resistor to V_{dd}
- Trireg**: models charge stored on a net

Verilog

CMOS VLSI Design

Slide 22

Verilog Value Types

- ❑ **Scalar:** (i.e. a single bit) may have values
 - 0: signal is driven to ground
 - 1: signal is driven high (typically to Vdd)
 - X: signal value is unknown or conflicted
 - Z: signal is “high impedance”
- ❑ **Sized numbers** written as `<number>'<base><digits>`
 - `<number>` is the number of digits
 - `<base>` is the base for the number representation
 - B or b: binary
 - O or o: octal
 - H or h: hexadecimal
 - D or d: decimal
 - `<digits>`: string of digits in the specified base notation
- ❑ **Unsigned numbers:** eliminate the `<number>`'

Verilog

CMOS VLSI Design

Slide 23

Value Examples

Table A.2 Constants				
Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	Binary	5	101
'b11	unsized	Binary	3	000000..00011
8'b11	8	Binary	3	00000011
8'b1010_1011	8	Binary	171	10101011
3'd6	3	Decimal	6	110
6'o42	6	Octal	34	100010
8'hAB	8	Hexadecimal	171	10101011
42	unsized	Decimal	42	0000...00101010


from W&H

Verilog

CMOS VLSI Design

Slide 24

MIPS Block Diagram

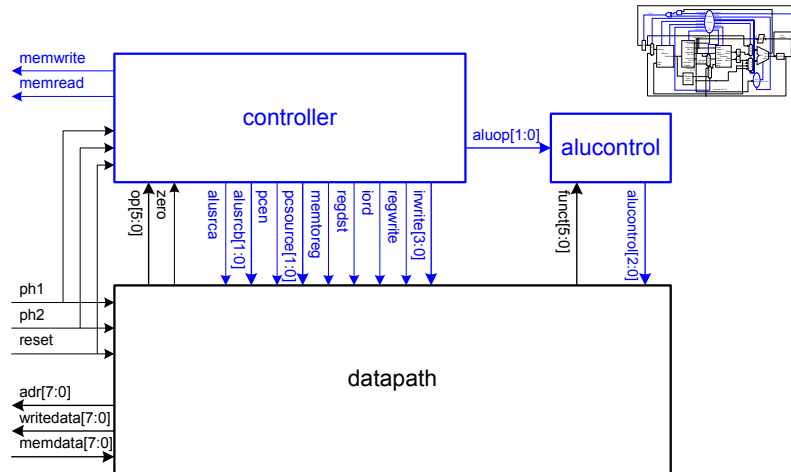

8bit MIPS

CMOS VLSI Design

Slide 25

High Level Verilog MIPS

```
// simplified MIPS processor
module mips #(parameter WIDTH = 8, REGBITS = 3)
    (input      clk, reset,
     input  [WIDTH-1:0] memdata,
     output   memread, memwrite,
     output  [WIDTH-1:0] adr, writedata);

    wire [31:0] instr;
    wire      zero, alusrca, memtoreg, iord, pccen, regwrite, regdst;
    wire [1:0] aluop, pcsource, alusrcb;
    wire [3:0] irwrite;
    wire [2:0] alucont;

    controller cont(clk, reset, instr[31:26], zero, memread, memwrite,
                   alusrca, memtoreg, iord, pccen, regwrite, regdst,
                   pcsource, alusrcb, aluop, irwrite);

    alucontrol ac(aluop, instr[5:0], alucont);

    datapath dp
    #(WIDTH, REGBITS)
    dp(clk, reset, memdata, alusrca, memtoreg, iord, pccen,
       regwrite, regdst, pcsource, alusrcb, irwrite, alucont,
       zero, instr, adr, writedata);

endmodule
```

Verilog

CMOS VLSI Design

Slide 26

Verilog Execution Model

Verilog Execution Model (1)

- ❑ Module definitions define
 - **Input** and **output ports** that can be wired to other module
 - **Behavior**: What happens in any instance when actual inputs change
- ❑ Model construction defines multiple **instances** of modules
 - How they are wired together
 - What to do “at time 0”

Verilog Execution Model (2)


- ❑ At any point in time
 - Compute values for all expressions that have been “activated”
 - Tag with time when changes should happen
 - Sort updates by time
- ❑ To advance to next step
 - Find updates with smallest time – make that the “current time”
 - Apply all updates
 - See (via appropriate netlists) which circuits see changes in inputs
 - Compute new values, tag the updates, and repeat

Verilog

CMOS VLSI Design

Slide 29

Discrete Event Execution

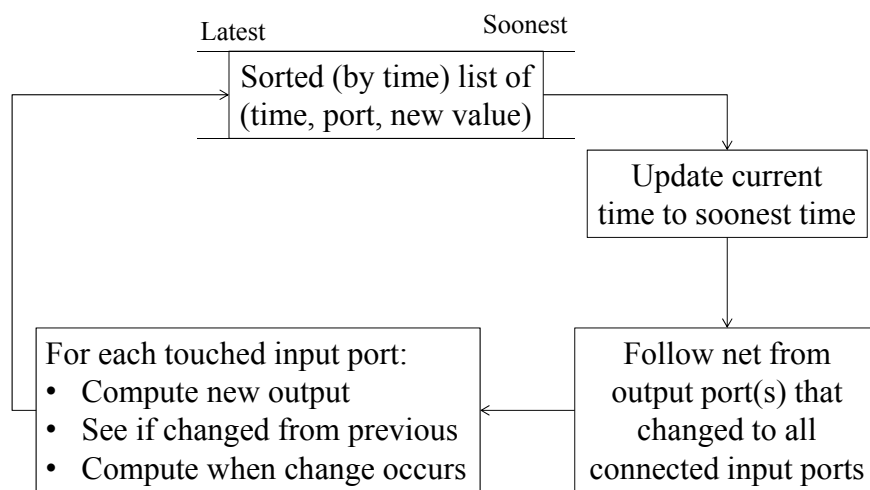

Verilog

CMOS VLSI Design

Slide 30

Verilog Behavioral Models & Expressions

Verilog

CMOS VLSI Design

Slide 31

Behavioral Models in Verilog

- ❑ Normal Purpose:
 - Simplify design process for “simple” logic
 - ***ESPECIALLY STATE MACHINES***
 - Avoid doing detailed structural design early in the design cycle
- ❑ Behavioral models act just like structural
 - Mixed model designs can be simulated simply
- ❑ Tools exist for **synthesizing** a structural design from behavior module

Verilog

CMOS VLSI Design

Slide 32

A Behavioral Module

```
module <module-name> (<port-list>);  
  
<declarations>  
  
assign #<delay> <net-name> = <expression>;  
  
endmodule
```

repeated multiple times

Distributing Signals: Nets

- **Net**: changes value whenever circuit driving it changes
 - Carries a signal
 - Most common – a **wire**
- **assign** #<delay> <net-name> = <expression>;
 - **Any change in expression changes value assigned to net**
 - <expression>: functional combination of constants and other signals
 - <net-name>: name of net that “tracks” value of expression
 - #<delay>: optional “delay” from time expression changes until time net signal changes

Operators in Expressions

Symbol	Meaning	Precedence
~	NOT	Highest
*, /, %	MUL, DIV, MODULO	
+, -	PLUS, MINUS	
<<, >>	Logical Left/Right Shift	
<<<, >>>	Arithmetic Left/Right Shift	
<, <=, >, >=	Relative Comparison	
==, !=	Equality Comparison	
&, ~&	AND, NAND	
^, ~^	XOR, XNOR	
, ~	OR, NOR	
?:	Conditional	Lowest

from W&H

Verilog

CMOS VLSI Design

Slide 35


Motivating Example

```
module fulladder(input a, b, c,
                output s, cout);
```

```
    Xor2      sum_1(a, b, s1);
    Xor2      sum_2(s1, c, s);
    carry     c1(a, b, c, cout);
endmodule
```

```
module carry(input a, b, c,
            output cout)
```

```
    assign cout = (a&b) | (a&c) | (b&c);
endmodule
```

 

Which is:

- Structural?
- Behavioral?


Verilog

CMOS VLSI Design

Slide 36

Example: Carry Logic – Standard Cell Gates

□ `assign cout = (a&b) | (a&c) | (b&c);`

 


Verilog

CMOS VLSI Design

Slide 37

Example: Carry Logic - Transistors

□ `assign cout = (a&b) | (a&c) | (b&c);`

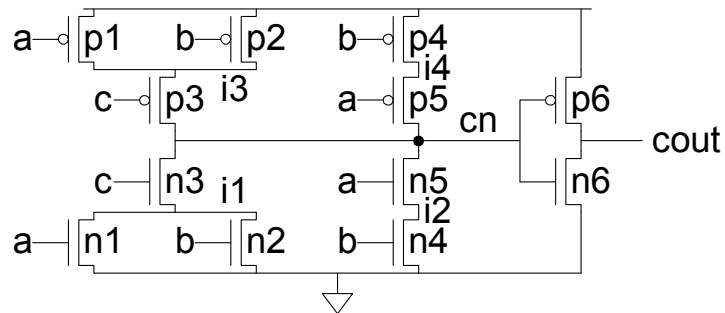


Verilog

CMOS VLSI Design

Slide 38

MIPS Datapath

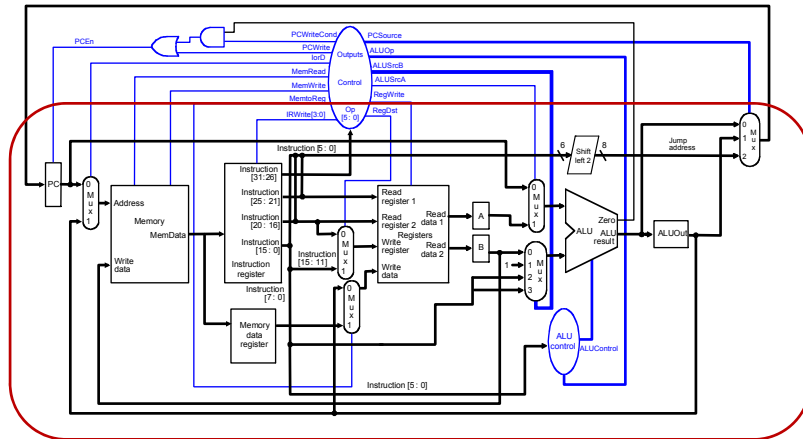- ❑ Multicycle μ architecture from Patterson & Hennessy




8bit MIPS

CMOS VLSI Design

Slide 39

Standard Cell Library

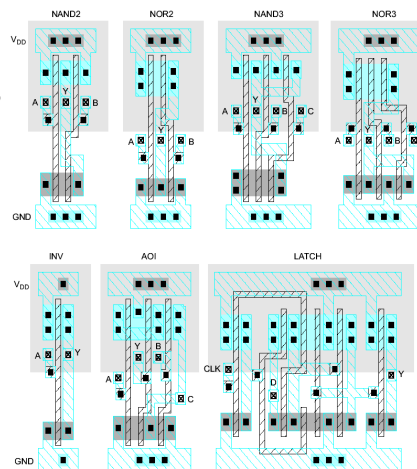- ❑ Uniform cell height
- ❑ Uniform well height
- ❑ M1 V_{DD} and GND rails
- ❑ M2 Access to I/Os
- ❑ Well / substrate taps
- ❑ Exploits regularity




8bit MIPS

CMOS VLSI Design

Slide 40

Slice Plans

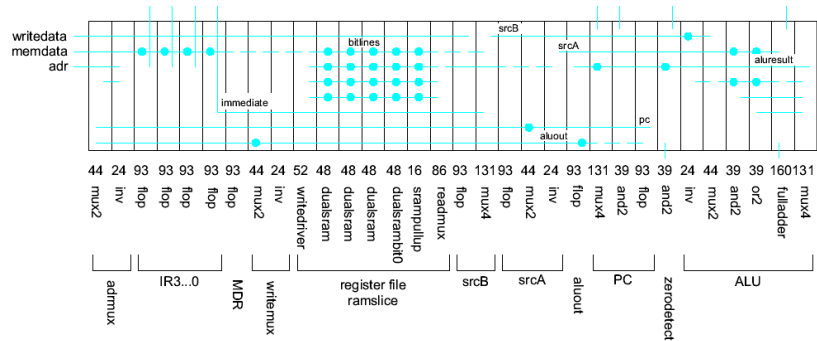- ❑ Slice plan for bitslice
 - Cell ordering, dimensions, wiring tracks
 - Arrange cells for wiring locality




8bit MIPS

CMOS VLSI Design

Slide 41

MIPS Datapath

 - ❑ 8-bit datapath built from 8 bitslices (regularity)
- ❑ Zipper at top drives control signals to datapath



8bit MIPS

CMOS VLSI Design

Slide 42

MIPS Verilog DataPath (1)

```

module datapath #(parameter WIDTH = 8, REGBITS = 3)
    (input      clk, reset,
     input  [WIDTH-1:0] memdata,
     input      alusrca, memtoreg, iord, pcen,
     regwrite, regdst,
     input  [1:0]    pcsource, alusrcb,
     input  [3:0]    irwrite,
     input  [2:0]    alucont,
     output         zero,
     output [31:0]   instr,
     output [WIDTH-1:0] adr, writedata);

    // size of the parameters must be changed to match the WIDTH parameter
    parameter CONST_ZERO = 8'b0;
    parameter CONST_ONE  = 8'b1;

    wire [REGBITS-1:0] ra1, ra2, wa;
    wire [WIDTH-1:0] pc, nextpc, md, rd1, rd2, wd, a, src1, src2, aluresult,
                aluout, constx4;

    // shift left constant field by 2
    assign constx4 = {instr[WIDTH-3:0],2'b00};

    // register file address fields
    assign ra1 = instr[REGBITS+20:21];
    assign ra2 = instr[REGBITS+15:16];
    mux2      #(REGBITS) regmux(instr[REGBITS+15:16], instr[REGBITS+10:11],
    regdst, wa);

```

Verilog

CMOS VLSI Design

Slide 43

MIPS Verilog Data Path (2)

```

    // independent of bit width, load instruction into four 8-bit registers
    over four cycles
    flopen    #(8)    ir0(clk, irwrite[0], memdata[7:0], instr[7:0]);
    flopen    #(8)    ir1(clk, irwrite[1], memdata[7:0], instr[15:8]);
    flopen    #(8)    ir2(clk, irwrite[2], memdata[7:0], instr[23:16]);
    flopen    #(8)    ir3(clk, irwrite[3], memdata[7:0], instr[31:24]);

    // datapath
    flopenr   #(WIDTH) pcreg(clk, reset, pcen, nextpc, pc);
    flop      #(WIDTH) mdr(clk, memdata, md);
    flop      #(WIDTH) areg(clk, rd1, a);
    flop      #(WIDTH) wrd(clk, rd2, writedata);
    flop      #(WIDTH) res(clk, aluresult, aluout);
    mux2      #(WIDTH) adrmux(pc, aluout, iord, adr);
    mux2      #(WIDTH) srclmux(pc, a, alusrca, src1);
    mux4      #(WIDTH) src2mux(writedata, CONST_ONE, instr[WIDTH-1:0],
    constx4, alusrcb, src2);
    mux4      #(WIDTH) pcmux(aluresult, aluout, constx4, CONST_ZERO,
    pcsource, nextpc);
    mux2      #(WIDTH) wdmux(aluout, md, memtoreg, wd);
    regfile   #(WIDTH,REGBITS) rf(clk, regwrite, ra1, ra2, wa, wd, rd1,
    rd2);
    alu       #(WIDTH) alunit(src1, src2, alucont, aluresult);
    zerodetect #(WIDTH) zd(aluresult, zero);
endmodule

```


Verilog

CMOS VLSI Design

Slide 44

MIPS ALU

 - Arithmetic / Logic Unit is part of bitslice



8bit MIPS

CMOS VLSI Design

Slide 45

Behavioral ALU

```
module alu #(parameter WIDTH = 8)
    (input [WIDTH-1:0] a, b,
    input [2:0] alucont,
    output reg [WIDTH-1:0] result);

    wire [WIDTH-1:0] b2, sum, slt;

    assign b2 = alucont[2] ? ~b:b;
    assign sum = a + b2 + alucont[2];
    // slt should be 1 if most significant bit of sum is 1
    assign slt = sum[WIDTH-1];

    always@(*)
        case(alucont[1:0])
            2'b00: result <= a & b;
            2'b01: result <= a | b;
            2'b10: result <= sum;
            2'b11: result <= slt;
        endcase
endmodule
```

Verilog

CMOS VLSI Design

Slide 46

Verilog Procedural Assignments

Continuous Assignments

- ❑ `assign` statements are “continuous”
- ❑ Written once, executed “continuously”
- ❑ Any changes in right hand side immediately reflected in left-hand signal
 - Delayed in time perhaps by `delay`
- ❑ If multiple assigns in a block,
 - execution is order independent

Procedural Assignments

- ❑ Sometime we want to execute statements **procedurally** (like a C program), i.e.
 - Start statements at some point in time
 - And then in some order
 - Especially important for controlling registers
- ❑ Two kinds of such behavior
 - **Single pass behavior** is executed only once
 - At initialization
 - **Cyclic behavior** is triggered whenever “something” happens
 - Where “something” can be defined in advance
- ❑ Need **registers** to capture values between changes

Verilog

CMOS VLSI Design

Slide 49

Registers

- ❑ Verilog **registers** much like C variables
 - Once assigned a value, they keep it
 - Until another value is assigned
- ❑ Defined by: **reg** [*<msb>:<lsb>*] *<reg-name>*;
 - If no [:] then default size is 1 bit
 - Initial value is “x”
- ❑ Typically assignments tied into events like clocks

Verilog

CMOS VLSI Design

Slide 50

Procedural Assignments

$\langle \text{reg-name} \rangle = \langle \text{expression} \rangle;$


- ❑ Note: no “assign”
- ❑ When statement executed, register takes on value from expression
 - Actually an update event is scheduled
- ❑ Update event is done BEFORE next statement in program order

Verilog

CMOS VLSI Design

Slide 51

A Level-Sensitive D Latch

 

```
module D_latch(input D, CLK, output Q);  
  
    Q = CLK ? D : Q;  
  
endmodule
```

Verilog

CMOS VLSI Design

Slide 52

A D Latch with a Reset

```
module D_latch_wReset(input D, CLK, Reset,
                    output Q);

Q = Reset ? 0 (CLK ? D : Q);

endmodule
```

Verilog

CMOS VLSI Design

Slide 53

Program Blocks

- ❑ Often more than 1 statement needs to be executed in a time-sensitive assignment
- ❑ Such statements grouped into **blocks**
 - `<statement>; ... <statement>;`
- ❑ **begin** `<statement-block>` **end**;
 - All statements in block are executed in order
 - i.e. one at a time top to bottom
 - Assignment statements within block are said to be **blocking assignments**
 - Next one cannot start until last completes
- ❑ **fork** `<statement-block>` **join**;
 - All statements in block are executed in parallel
 - i.e. in any order

Verilog

CMOS VLSI Design

Slide 54

Single Execution Behavior

- ❑ Execute *only* at specific time, i.e. time=0
- ❑ Typically used by test benches for startup

```
initial <statement>;
```

- ❑ Example:

```
initial begin
  Reset = 0;
  #10 Reset = 1;
  #5 Reset = 0;
end
```

What is the waveform?

Verilog

CMOS VLSI Design

Slide 55

Controlling Cyclic Behavior

- ❑ Statement to be executed at specific times
 - E.g. at clock pulses
- ❑ `always @(<sensitivity list>) <statement>`
- ❑ `@` is optional **event control operator**
- ❑ `<sensitivity-list>` is list of signal names
 - `@*` means use all nets & variables read by procedure's statements
- ❑ Whenever any one of signals in sensitivity-list changes, `<statement>` is executed
 - And only then
- ❑ What kind of change is immaterial, unless signal name preceded by:
 - **posedge**: execute only on a 0 to 1
 - **negedge**: execute only on a 1 to 0

Verilog

CMOS VLSI Design

Slide 56

Non-blocking Assignments

- ❑ Use of “<=“ instead of “=“ in assignment makes statement execute *concurrently* with later statements
`<register> <= <expression>;`

- left-hand side MUST be a register

- ❑ Order of such assignments is immaterial;
– They ALL HAPPEN AT ONCE!

- ❑ Better match to real circuits

```
always @(posedge clock)
```

```
begin
```

```
reg1 <= expr1;
```

```
reg2 <= expr2;
```

```
...
```

```
end
```

All expressions evaluated
at same time;
then all assignments happen
at same time

Verilog

CMOS VLSI Design

Slide 57

Example: Clock Generation

```
Reg clk;
```

```
always
```

```
begin
```

```
clk <= 1; schedules a change to clk “now”
```

```
# 5;
```

```
clk <= 0; schedules a change to clk  
in 5 time units
```

```
# 5;
```

```
end
```

Verilog

CMOS VLSI Design

Slide 58

Assignment Summary


- ❑ Continuous assignment:
 - `assign #<delay> <net-name> = <expression>`
- ❑ Procedural assignment:
 - `<register> = <expression>;`
- ❑ Non-blocking assignment:
 - `<register> <=> <expression>;`

Verilog

CMOS VLSI Design

Slide 59

Finite State Machines

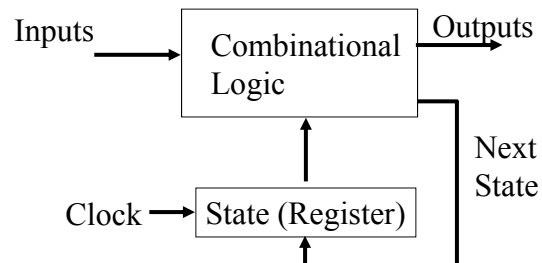


```
module FSM(input clock, In1, ...Inn, output O1, ...Om);
    reg state, next_state;
    always @(posedge clock)
    begin
        state <= next_state;
        ...
        Code that does something like next_state <= <expression>;
        ...
    end
end
```

Verilog

CMOS VLSI Design

Slide 60

Multicycle Controller

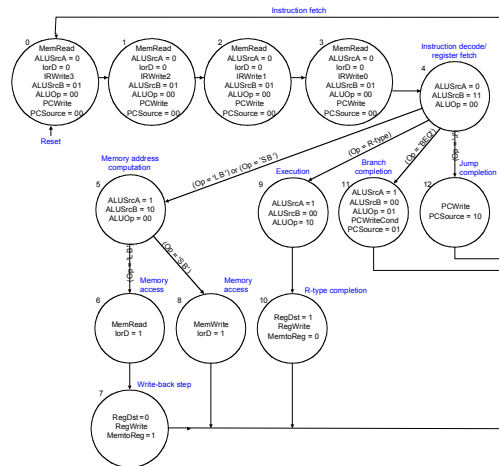

8bit MIPS

CMOS VLSI Design

Slide 61

MIPS VERILOG CONTROL LOGIC

```

module controller(input clk, reset,
                 input  [5:0] op,
                 input      zero,
                 output reg memread, memwrite, alusrcA, memtoReg, iord,
                 output      pcen,
                 output reg  regwrite, regdst,
                 output reg [1:0] psource, alusrcB, aluop,
                 output reg [3:0] irwrite);
    
```

- ❑ Next: list of constants to define machine states
- ❑ Then an “always” sensitive to rising edge of clock
 - Embedded case statement
 - One case per state
 - Determines what new state should be at end of this clock
- ❑ Then an “always” sensitive to any change in values
 - Embedded case statement
 - Each case specifies control signals to dataflow & memory

Verilog

CMOS VLSI Design

Slide 62

More Syntax

Memory

`reg <word-size> <memory-name> <mem-size>...<mem-size>;`

- ❑ `<word-size>` is [`<msb>:<lsb>`]
- ❑ `<mem-size>` is [`<low-index>:<high-index>`]
- ❑ Example: define register `d_array` as 2D array of 16 bit words

```
reg [15:0] d_array [0:127][0:255]
```
- ❑ Selecting a word from an array:
 - Assume `a_byte` is an 8 bit set of wires

```
a_byte = d_array[64][32][12:5];
```
 - takes 8 bits from 32nd column of 64th row

Other Verilog Constructs

- ❑ **Comments:**
 - **Single line:** `// ...`
 - **Block:** `/* */`
- ❑ **Identifiers:**
 - start with letter or `_`
 - follow by letters, digits, `_`, or `$`
 - case sensitive

If Statement

```
if (<expression>
    <then_statement>
else <else_statement>
end
```

- ❑ else is optional
- ❑ nesting permitted, as in else if

Case Statement

```
case (<expression>
    <case_item>: <case_item_statement>
    ...
    default: <case_item_statement>
endcase
```

- ❑ <case_item> is a constant that is matched against that from the <expression>
 - If match, then do the <case_item_statement>
 - And exit case statement after completion
 - If not, try next case
- ❑ default is optional for no matches

Verilog

CMOS VLSI Design

Slide 67

For Statement

```
for (<initial_assignment>;
    <condition-expression>;
    <update_statement>)
begin
<loop-statements>
end
```

- ❑ <initial_assignment> and <update_statement> are some form of assignment
- ❑ All iterations of <loop-statements> conceptually done AT SAME TIME

Verilog

CMOS VLSI Design

Slide 68

Other Loops

```
repeat (<expression>
begin
<loop-statements>
end

while (<condition>)
begin
<loop-statements>
end

wait (<expression>) <statement>
```

- ❑ All iterations of <loop-statements> conceptually done AT SAME TIME

Timescale

- ❑ ``timescale <time_unit>/<time_precision>`
 - <time_unit> and <time_precision> of form:
 - <number> <space> <unit>
 - with <unit> as **s ms us ns ps fs**
- ❑ From this point on:
 - for delays: 1 time unit = <time_unit>
 - for precision of internal time calculations: use <time_precision>

Module Instantiation Options

- ❑ Previously
`<module-type> <instance-name> (<list-of-signal-names>);`
- ❑ In place of `<list-of-signal-names>`, use list of
`.<port-name>(<net-name>)`
- ❑ Optionally add `#(<parameter_assignment_list>)` after
`<module-type>`
 - Associate values with parameters within module definition
 - Overwrites `parameter <name> = <value>` inside definition

Verilog

CMOS VLSI Design

Slide 71

More (See Quick Reference Card)

- ❑ Builtin modules: and, or, nand, nor, xor, xnor
 - One output (first argument)
 - One or more inputs (rest of arguments)
 - ❑ `$display` statement: verilog eqvt of printf
 - `$display (<format string>);`
 - (“ ... text ...”, `<list of var-names>`)
 - `%<format-code>` in text says how to format “next” var in list
 - `$time` is current time
 - executed as any other statement in a block
 - references variable values AS THEY ARE THEN
- see <http://www.hpcc.ecs.soton.ac.uk/hpci/tools/vlogref.pdf>

Verilog

CMOS VLSI Design

Slide 72

More Examples

Verilog

CMOS VLSI Design

Slide 73

Typical Design

- ❑ File with list of module definitions
- ❑ Typically first one is a **testbench**
 - Glues together other pieces in a way that allows appropriate operation to be demonstrated
 - Includes **initial code** to start up & reset system
 - Includes code to generate clocks & other common control signals

```
module TestBench(); \\ no ports
reg <in-list>; \\ all input ports to DUT
wire <out-list>; \\ all output ports from DUT

module Device_Under_Test(input <in-list>, output <outlist>);
...
endmodule;

initial begin
    code to change values of regs in <in-list>
end;


endmodule;
```

Verilog

CMOS VLSI Design

Slide 74

A Behavioral Full Adder

 

```

module fulladder(input a, b, cin, output s, cout);
  wire prop;
  assign prop = a ^ b;
  assign s = prop ^ cin;
  assign cout = ( a & b ) | (cin & ( a | b ));
endmodule

```


Note: "order" of *assigns* in code is irrelevant

Verilog

CMOS VLSI Design

Slide 75

Example: A 4 bit Shift Register

 

```

Module shiftreg(input E, clk, reset,
  output D, C, B, A);
  reg A, B, C, D; // note these output port defined to be regs
  always @(posedge clk or posedge reset)
  begin
    if (reset) begin A=0;B=0;C=0;D=0;E=0; end
    else begin
      A = B;
      B = C;
      C = D;
      D = E;
    end
  end
end

```


What happens if we reorder these?

Verilog

CMOS VLSI Design

Slide 76

Repeat Shift Register Example:

 

```

Module shiftreg(input E, clk, reset,
                output reg D, C, B, A);
    always @(posedge clk or posedge reset)
    begin
        if (reset) begin A<=0;B<=0;C<=0;D<=0;E<=0; end
        else begin
            A <= B;
            B <= C;
            C <= D;
            D <= E;
        end
    end
end
    
```

Note simplified syntax


Now what happens if we reorder these?

Verilog

CMOS VLSI Design

Slide 77

Finite State Machines

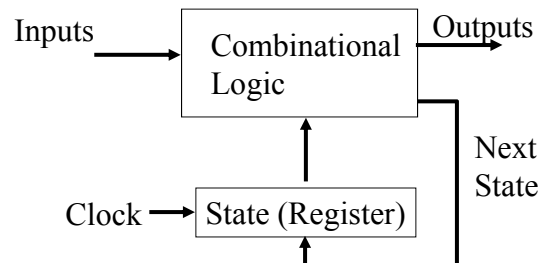

```

module FSM(input clock, In1, ...Inn, output O1, ...Om);
    reg state, next_state;
    parameter ... statei = 'bxxxx;
    always @(posedge clock)
    begin
        state <= next_state;
        case (state)
            ...
            statei: begin next_state<=statej; Ok <= ... end;
            ...
        end
    end
end
    
```

Verilog

CMOS VLSI Design

Slide 78